

# Gate-Level Minimization

section instructor:  
**Ufuk Çelikcan**

# Complexity of Digital Circuits

- Directly related to the complexity of the algebraic expression we use to build the circuit.
- Truth table
  - may lead to different implementations
  - Question: which one to use?
- Optimization techniques of algebraic expressions
  - So far, ad hoc.
  - Need more systematic (algorithmic) way
    - Karnaugh (K-) map technique
    - Quine-McCluskey
    - Espresso

# Two-Variable K-Map

- Two variables:  $x$  and  $y$

4 minterms:

- $m_0 = x'y'$        $\rightarrow 00$
- $m_1 = x'y$        $\rightarrow 01$
- $m_2 = xy'$        $\rightarrow 10$
- $m_3 = xy$        $\rightarrow 11$

	$y$		
		0	1
$x$	0	$m_0$	$m_1$
	1	$m_2$	$m_3$

	$y$		
		0	1
$x$	0	$x'y'$	$x'y$
	1	$xy'$	$xy$

# Example: Two-Variable K-Map

		y	
		0	1
x	0	1	1
	1	1	0

➤  $F = m_0 + m_1 + m_2 = x'y' + x'y + xy'$

➤  $F = \dots$

➤  $F = \dots$

➤  $F = \dots$

# Remember the Shortcuts

$$\blacktriangleright x + x = x \iff x \cdot x = x$$

$$\blacktriangleright x + 1 = 1 \iff x \cdot 0 = 0$$

$$\blacktriangleright x + xy = x \iff x \cdot xy = x \quad [\text{Absorption}]$$

$$\blacktriangleright (x + y)' = x' \cdot y' \iff (x \cdot y)' = x' + y' \quad [\text{DeMorgan}]$$

# Example: Two-Variable K-Map

		y	
		0	1
x	0	1	1
	1	1	0

➤  $F = m_0 + m_1 + m_2 = x'y' + x'y + xy'$

➤  $F = \dots$

➤  $F = \dots$

➤  $F = \dots$

➤  $F = x' + y'$

- We can do the same optimization by combining adjacent cells.

# Three-Variable K-Map

		yz			
		00	01	11	10
x	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$

- Adjacent squares: they **differ by only one variable**, which is primed in one square and not primed in the other
  - $m_2 \leftrightarrow m_6$ ,  $m_3 \leftrightarrow m_7$
  - $m_2 \leftrightarrow m_0$ ,  $m_6 \leftrightarrow m_4$

# Example: Three-Variable K-Map

- $F_1(x, y, z) = \sum (2, 3, 4, 5)$

x \ yz	00	01	11	10
0				
1				

- $F_1(x, y, z) =$

- $F_2(x, y, z) = \sum (3, 4, 6, 7)$

x \ yz	00	01	11	10
0				
1				

- $F_2(x, y, z) =$



# Example: Three-Variable K-Map

- $F_1(x, y, z) = \sum (2, 3, 4, 5)$

		yz			
		00	01	11	10
x	0	0	0	1	1
	1	1	1	0	0

- $F_1(x, y, z) =$

- $F_2(x, y, z) = \sum (3, 4, 6, 7)$

		yz			
		00	01	11	10
x	0	0	0	1	0
	1	1	0	1	1

- $F_2(x, y, z) =$

# Example: Three-Variable K-Map

- $F_1(x, y, z) = \sum (2, 3, 4, 5)$

		yz			
		00	01	11	10
x	0	0	0	1	1
	1	1	1	0	0

- $F_1(x, y, z) = xy' + x'y$

- $F_2(x, y, z) = \sum (3, 4, 6, 7)$

		yz			
		00	01	11	10
x	0	0	0	1	0
	1	1	0	1	1


- $F_2(x, y, z) = xz' + yz$

# In 3-Variable Karnaugh Maps

- 1 alone square represents one minterm with 3 literals
- 2 adjacent squares represent a term with 2 literals
- 4 adjacent squares represent a term with 1 literal
- 8 adjacent squares produce a function that is always equal to 1.

# Example

- $F_1(x, y, z) = \sum (0, 2, 4, 5, 6)$

 

$$F_1(x, y, z) =$$

# Example

- $F_1(x, y, z) = \sum (0, 2, 4, 5, 6)$

		yz			
		00	01	11	10
x	0	1	0	0	1
	1	1	1	0	1

$$F_1(x, y, z) =$$

# Example

- $F_1(x, y, z) = \sum (0, 2, 4, 5, 6)$

x	yz			
	00	01	11	10
0	1	0	0	1
1	1	1	0	1

$$F_1(x, y, z) =$$

# Finding Sum of Minterms

- If a function is not expressed in sum of minterms form, it is possible to get it using K-maps
  - Example:  $F(x, y, z) = x'z + x'y + xy'z + yz$

x \ yz	00	01	11	10
0				
1				

# Finding Sum of Minterms

- If a function is not expressed in sum of minterms form, it is possible to get it using K-maps
  - Example:  $F(x, y, z) = x'z + x'y + xy'z + yz$


x \ yz	00	01	11	10
0				
1				

$$F(x, y, z) = x'y'z + x'yz + x'yz' + xy'z + xyz$$


 
# Four-Variable K-Map

- Four variables:  $x, y, z, t$ 
  - 4 literals
  - 16 minterms



# Example: Four-Variable K-Map

$$F(x,y,z,t) = \Sigma (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$

zt \ xy	00	01	11	10
00				
01				
11				
10				

$$F(x,y,z,t) =$$

# Example: Four-Variable K-Map


$$F(x,y,z,t) = \Sigma (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$

zt \ xy	00	01	11	10
00	1	1	0	1
01	1	1	0	1
11	1	1	0	1
10	1	1	0	0

$$F(x,y,z,t) =$$
 
# Example: Four-Variable K-Map

$$F(x,y,z,t) = \Sigma (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$



$$F(x,y,z,t) =$$

# Example: Four-Variable K-Map

- $F(x,y,z,t) = x'y'z' + y'zt' + x'yz't' + xy'z'$

zt \ xy	00	01	11	10
00				
01				
11				
10				

- $F(x,y,z,t) =$

# Example: Four-Variable K-Map

- $F(x,y,z,t) = x'y'z' + y'zt' + x'yz't' + xy'z'$

zt \ xy	00	01	11	10
00	1	1	0	1
01	0	0	0	1
11	0	0	0	0
10	1	1	0	1

- $F(x,y,z,t) =$

# Example: Four-Variable K-Map

- $F(x,y,z,t) = x'y'z' + y'zt' + x'yz't' + xy'z'$

zt \ xy	00	01	11	10
00	1	1	0	1
01	0	0	0	1
11	0	0	0	0
10	1	1	0	1

- $F(x,y,z,t) =$

# Prime Implicants

- Prime Implicant: is a product term obtained by combining maximum possible number of adjacent squares in the map
- If a minterm can be covered by only one prime implicant, that prime implicant is said to be an **essential prime implicant**.
  - A single 1 on the map represents a prime implicant if it is not adjacent to any other 1's.
  - Two adjacent 1's form a prime implicant, provided that they are not within a group of four adjacent 1's.
  - So on



# Example: Prime Implicants

- $F(x,y,z,t) = \Sigma (0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$

		zt			
		00	01	11	10
xy	00				
	01				
	11				
	10				

# Example: Prime Implicants

- $F(x,y,z,t) = \Sigma (0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$

zt xy	00	01	11	10
00	1	0	1	1
01	0	1	1	0
11	0	1	1	0
10	1	1	1	1

# Example: Prime Implicants

- $F(x,y,z,t) = \Sigma (0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$

		zt			
		00	01	11	10
xy	00	1	0	1	1
	01	0	1	1	0
	11	0	1	1	0
	10	1	1	1	1

$$F(x,y,z,t) = y't' + yt + xy' + zt$$

- Which ones are the **essential prime implicants**?

# Example: Prime Implicants

- $F(x,y,z,t) = \Sigma (0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$

A 4x4 Karnaugh map for the function  $F(x,y,z,t) = \Sigma (0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$ . The vertical axis is labeled 'zt' and the horizontal axis is labeled 'xy'. The rows are labeled 00, 01, 11, 10 and the columns are labeled 00, 01, 11, 10. The map contains 1s in the following cells: (00,00), (00,10), (01,01), (01,11), (11,01), (11,11), (10,00), (10,01), (10,11), (10,10). A red box highlights the 2x2 block of 1s in the middle (rows 01 and 11, columns 01 and 11). Four red curved lines highlight other prime implicants: a vertical line through the first column (00), a vertical line through the last column (10), a horizontal line through the first row (00), and a horizontal line through the last row (10).

zt \ xy	00	01	11	10
00	1	0	1	1
01	0	1	1	0
11	0	1	1	0
10	1	1	1	1

- Why are these the **essential prime implicants**?

# Example: Prime Implicants

- $F(x,y,z,t) = \Sigma (0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$

		zt			
		00	01	11	10
xy	00	1	0	1	1
	01	0	1	1	0
	11	0	1	1	0
	10	1	1	1	1

		zt			
		00	01	11	10
xy	00	$m_0$	$m_1$	$m_3$	$m_2$
	01	$m_4$	$m_5$	$m_7$	$m_6$
	11	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
	10	$m_8$	$m_9$	$m_{11}$	$m_{10}$

- $y't'$  - essential since  $m_0$  is covered only in it
- $yt$  - essential since  $m_5$  is covered only in it
- They together cover  $m_0, m_2, m_8, m_{10}, m_5, m_7, m_{13}, m_{15}$

# Example: Prime Implicants

zt		xy			
		00	01	11	10
00	1	0	1	1	
01	0	1	1	0	
11	0	1	1	0	
10	1	1	1	1	

zt		xy			
		00	01	11	10
00	$m_0$	$m_1$	$m_3$	$m_2$	
01	$m_4$	$m_5$	$m_7$	$m_6$	
11	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$	
10	$m_8$	$m_9$	$m_{11}$	$m_{10}$	

- $m_3, m_9, m_{11}$  are not yet covered.
- How do we cover them?
- There is actually more than one way.

# Example: Prime Implicants

zt \ xy	00	01	11	10
00	1	0	1	1
01	0	1	1	0
11	0	1	1	0
10	1	1	1	1

Diagram illustrating prime implicants on a Karnaugh map. The map is a 4x4 grid with rows labeled 00, 01, 11, 10 and columns labeled 00, 01, 11, 10. The top-left cell is labeled 'zt' and the bottom-left cell is labeled 'xy'. The map contains several prime implicants: a blue circle around the cell (11, 11) labeled '3'; a blue rectangle around the cells (10, 00), (10, 01), (10, 11), and (10, 10) labeled '4'; a brown rectangle around the cells (00, 11), (01, 11), (11, 11), and (10, 11) labeled '2'; a brown rectangle around the cells (00, 11), (00, 10), (01, 11), and (01, 10) labeled '1'; and a brown rectangle around the cells (11, 11), (11, 10), (10, 11), and (10, 10) labeled '1'. There are also diagonal lines drawn across the map.

- Both  $y'z$  and  $zt$  covers  $m_3$  and  $m_{11}$ .
- $m_9$  can be covered in two different prime implicants:
  - $xt$  or  $xy'$
- $m_3, m_{11} \rightarrow zt$  or  $y'z$
- $m_9 \rightarrow xy'$  or  $xt$

# Example: Prime Implicants

- $F(x, y, z, t) = yt + y't' + zt + xt$  or
- $F(x, y, z, t) = yt + y't' + zt + xy'$  or
- $F(x, y, z, t) = yt + y't' + y'z + xt$  or
- $F(x, y, z, t) = yt + y't' + y'z + xy'$
- Therefore, what to do
  1. Find out all the essential prime implicants
  2. Then find the other prime implicants that cover the minterms that are not covered by the essential prime implicants. There are more than one way to choose those.
  3. Simplified expression is the logical sum of the essential implicants plus the other implicants



# Five-Variable Map

- Downside:
  - Karnaugh maps with more than four variables are not simple to use anymore.
  - 5 variables  $\rightarrow$  32 squares, 6 variables  $\rightarrow$  64 squares
  - Somewhat more practical way for  $F(x, y, z, t, w)$  :

		tw			
		00	01	11	10
yz	00	$m_0$	$m_1$	$m_3$	$m_2$
	01	$m_4$	$m_5$	$m_7$	$m_6$
	11	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
	10	$m_8$	$m_9$	$m_{11}$	$m_{10}$

$x = 0$

		tw			
		00	01	11	10
yz	00	$m_{16}$	$m_{17}$	$m_{19}$	$m_{18}$
	01	$m_{20}$	$m_{21}$	$m_{23}$	$m_{22}$
	11	$m_{28}$	$m_{29}$	$m_{31}$	$m_{30}$
	10	$m_{24}$	$m_{25}$	$m_{27}$	$m_{26}$

$x = 1$

# Many-Variable Maps

- Adjacency:
  - Each square in the  $x = 0$  map is adjacent to the corresponding square in the  $x = 1$  map.
  - For example,  $m_4 \rightarrow m_{20}$  and  $m_{15} \rightarrow m_{31}$
- 6-variables: Use **four** 4-variable maps to obtain 64 squares required for six variable optimization
- **Alternative way:** Can use computer programs
  - Quine-McCluskey method
  - Espresso method

# Example: Five-Variable Map

$$F(x, y, z, t, w) = \Sigma (0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31)$$

tw \ yz	00	01	11	10
00				
01				
11				
10				

$x = 0$

tw \ yz	00	01	11	10
00				
01				
11				
10				

$x = 1$

•  $F(x, y, z, t, w) =$

# Example: Five-Variable Map

$$F(x, y, z, t, w) = \Sigma (0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31)$$

yz \ tw	00	01	11	10
00	1			1
01	1			1
11		1		
10		1		

$x = 0$

yz \ tw	00	01	11	10
00				
01		1	1	
11		1	1	
10		1		

$x = 1$

•  $F(x, y, z, t, w) =$

# Example: Five-Variable Map

$$F(x, y, z, t, w) = \Sigma (0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31)$$

	tw			
yz	00	01	11	10
00	1			1
01	1			1
11		1		
10		1		

$x = 0$

	tw			
yz	00	01	11	10
00				
01		1	1	
11		1	1	
10		1		

$x = 1$

•  $F(x, y, z, t, w) =$

# Product of Sums Simplification

- So far
  - simplified expressions from Karnaugh maps are in sum of products form.
- Simplified product of sums can also be derived from Karnaugh maps.
- Method:
  - A square with 1 actually represents a “minterm”
  - Similarly an empty square (a square with 0) represents a “maxterm”.
  - Treat the 0's in the same manner as we treat 1's
  - The result is a simplified expression in product of sums form.

# Example: Product of Sums


- $F(x, y, z, t) = \Sigma (0, 1, 2, 5, 8, 9, 10)$ 
  - Simplify this function in
    - a. sum of products
    - b. product of sums

zt \ xy	00	01	11	10
00	1	1		1
01		1		
11				
10	1	1		1

$$F(x, y, z, t) =$$
 
# Example: Product of Sums

- $F(x, y, z, t) = \Sigma (0, 1, 2, 5, 8, 9, 10)$ 
  - Simplify this function in
    - a. sum of products
    - b. product of sums




$$F(x, y, z, t) =$$


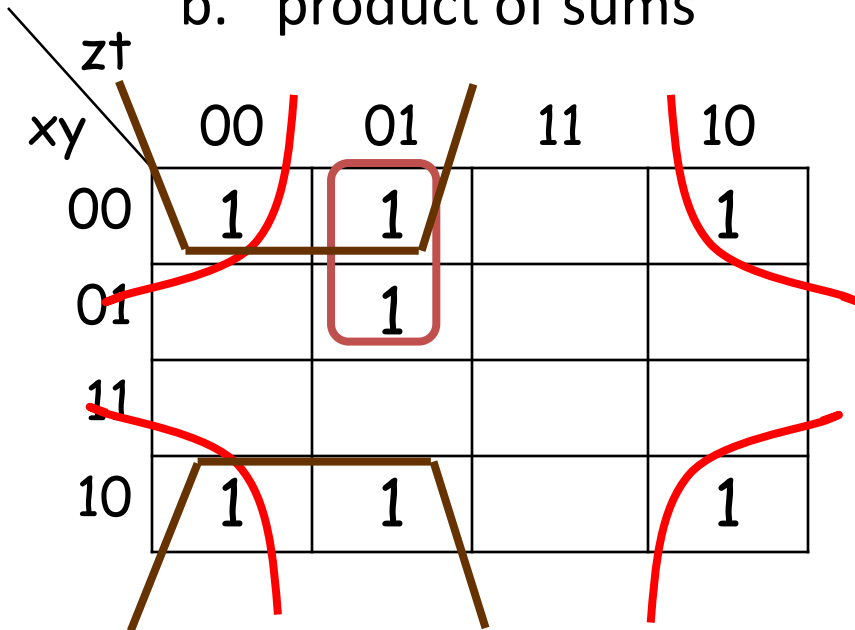
# Example: Product of Sums

- $F(x, y, z, t) = \Sigma (0, 1, 2, 5, 8, 9, 10)$ 
  - Simplify this function in
    - a. sum of products
    - b. product of sums



$$F(x, y, z, t) = y't' + y'z' + x'z't$$

# Example: Product of Sums

1. Find  $F'(x,y,z,t)$  in Sum of Products form by grouping 0's
2. Apply DeMorgan's theorem to  $F'$  (use dual theorem) to find  $F$  in Product of Sums form

zt \ xy	00	01	11	10
00	1	1	0	1
01	0	1	0	0
11	0	0	0	0
10	1	1	0	1

# Example: Product of Sums

1. Find  $F'(x,y,z,t)$  in Sum of Products form by grouping 0's
2. Apply DeMorgan's theorem to  $F'$  (use dual theorem) to find  $F$  in Product of Sums form

zt \ xy	00	01	11	10
00	1	1	0	1
01	0	1	0	0
11	0	0	0	0
10	1	1	0	1

# Example: Product of Sums

1. Find  $F'(x,y,z,t)$  in Sum of Products form by grouping 0's
2. Apply DeMorgan's theorem to  $F'$  (use dual theorem) to find  $F$  in Product of Sums form

A Karnaugh map for the function  $F'(x,y,z,t)$  with variables  $x, y, z, t$ . The map is a 4x4 grid with rows labeled  $xy$  (00, 01, 11, 10) and columns labeled  $zt$  (00, 01, 11, 10). The cells contain values: 1 (purple) and 0 (black). A green box groups the 0s at  $(xy, zt) = (00, 11), (01, 11), (11, 11), (10, 11)$ . A red box groups the 0s at  $(xy, zt) = (11, 00), (11, 01), (11, 11), (11, 10)$ . Brown lines group the 1s at  $(xy, zt) = (00, 00), (01, 00), (10, 00), (10, 10)$  and  $(xy, zt) = (00, 01), (01, 01), (10, 01), (10, 10)$ .

$xy \backslash zt$	00	01	11	10
00	1	1	0	1
01	0	1	0	0
11	0	0	0	0
10	1	1	0	1

$$F' = yt' + zt + xy$$

# Example: Product of Sums


1. Find  $F'(x,y,z,t)$  in Sum of Products form by grouping 0's
2. Apply DeMorgan's theorem to  $F'$  (use dual theorem) to find  $F$  in Product of Sums form

A Karnaugh map for the function  $F(x,y,z,t)$  with variables  $x, y, z, t$ . The map is a 4x4 grid with rows labeled  $xy$  (00, 01, 11, 10) and columns labeled  $zt$  (00, 01, 11, 10). The cells contain values: (00,00)=1, (00,01)=1, (00,11)=0, (00,10)=1; (01,00)=0, (01,01)=1, (01,11)=0, (01,10)=0; (11,00)=0, (11,01)=0, (11,11)=0, (11,10)=0; (10,00)=1, (10,01)=1, (10,11)=0, (10,10)=1. A green box groups the 0's at (00,11), (01,11), and (10,11). A red box groups the 0's at (11,00), (11,01), (11,11), and (11,10). Brown lines connect the 1's at (00,00), (00,01), (00,10), (01,00), (01,01), (10,00), (10,01), (10,10), and (10,10) to the corresponding terms in the final expression.


$xy \backslash zt$	00	01	11	10
00	1	1	0	1
01	0	1	0	0
11	0	0	0	0
10	1	1	0	1

$$F(x,y,z,t) = (y'+t)(z'+t')(x'+y')$$

# Example: Product of Sums

 

 $F(x,y,z,t) = y't' + y'z' + x'z't'$ : sum of products implementation



$F = (y' + t)(x' + y')(z' + t')$ : product of sums implementation

# Product of Maxterms

- If the function is originally expressed in the product of maxterms canonical form, the procedure is also valid
- Example:

$$- F(x, y, z) = \Pi (0, 2, 5, 7)$$

x \ yz	00	01	11	10
0				
1				

$$F(x, y, z) =$$

# Product of Maxterms

- If the function is originally expressed in the product of maxterms canonical form, the procedure is also valid
- Example:
  - $F(x, y, z) = \Pi (0, 2, 5, 7)$

		yz			
		00	01	11	10
x	0	0			0
	1		0	0	

$F(x, y, z) =$



# Product of Maxterms

- If the function is originally expressed in the product of maxterms canonical form, the procedure is also valid
- Example:

$$- F(x, y, z) = \Pi (0, 2, 5, 7)$$

x \ yz	00	01	11	10
0	0			0
1		0	0	

$$F(x, y, z) =$$

$$F(x, y, z) = x'z + xz'$$

# Product of Sums

- To enter a function  $F$ , expressed in product of sums, in the map
  1. take its complement,  $F'$
  2. Find the squares corresponding to the terms in  $F'$ ,
  3. Fill these square with 0's and others with 1's.
- Example:
  - $F(x, y, z, t) = (x' + y' + z')(y + t)$
  - $F'(x, y, z, t) =$

# Product of Sums

- To enter a function  $F$ , expressed in product of sums, in the map
  1. take its complement,  $F'$
  2. Find the squares corresponding to the terms in  $F'$ ,
  3. Fill these square with 0's and others with 1's.

- Example:

- $F(x, y, z, t) = (x' + y' + z')(y + t)$

- $F'(x, y, z, t) =$

		zt			
		00	01	11	10
xy	00	0			0
	01				
	11			0	0
	10	0			0

# Don't Care Conditions

- Some functions are not defined for certain input combinations
  - Such functions are referred to as incompletely specified functions
  - **therefore, the corresponding output values do not have to be defined**
  - This may significantly reduce the circuit complexity
  - Example: A circuit that takes the 10's complement of decimal digits

# Unspecified Minterms

- For unspecified minterms, we do not care what the value the function produces.
- Unspecified minterms of a function are called don't care conditions.
- We use “X” symbol to represent them in Karnaugh map.
- Useful for further simplification
- **The symbol X's in the map can be taken as 0 or 1 to make the Boolean expression even more simplified**

# Example: Don't Care Conditions

- $F(x, y, z, t) = \Sigma(1, 3, 7, 11, 15)$  – function
- $d(x, y, z, t) = \Sigma(0, 2, 5)$  – don't care conditions

		zt			
		00	01	11	10
xy	00	X	1	1	X
	01	0	X	1	0
	11	0	0	1	0
	10	0	0	1	0

$F =$

$F_1 =$

or

$F_2 =$

# Example: Don't Care Conditions

- $F(x, y, z, t) = \Sigma(1, 3, 7, 11, 15)$  – function
- $d(x, y, z, t) = \Sigma(0, 2, 5)$  – don't care conditions

zt \ xy	00	01	11	10
00	X	1	1	X
01	0	X	1	0
11	0	0	1	0
10	0	0	1	0

$F =$

$F_1 =$

or

$F_2 =$

# Example: Don't Care Conditions

- $F_1 = zt + x'y' = \Sigma(0, 1, 2, 3, 7, 11, 15)$
- $F_2 = zt + x't = \Sigma(1, 3, 5, 7, 11, 15)$
- The two functions are algebraically unequal
  - But as far as the function  $F$  is concerned: both functions are acceptable
- Look at the simplified product of sums expression for the same function  $F$ .

		zt			
		00	01	11	10
xy	00	X	1	1	X
	01	0	X	1	0
	11	0	0	1	0
	10	0	0	1	0

$F' =$

$F =$



# Quine-McCluskey Method

- Better than kmap for computers because a computer cant break down a graphical thing like K-map, but it can easily solve by QM
- It is functionally identical to Karnaugh mapping,
- but the tabular form makes it more efficient for use in computer algorithms,
- and it also gives a deterministic way to check that the minimal form of a Boolean function has been reached.
- It is sometimes referred to as the tabulation method.

# Quine-McCluskey Method

- $F(x_1, x_2, x_3, x_4) = \sum 2, 4, 6, 8, 9, 10, 12, 13, 15$

<b>mi</b>	<b>x1</b>	<b>x2</b>	<b>x3</b>	<b>x4</b>
<b>2</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>
<b>4</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>
<b>8</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>
<b>6</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>
<b>9</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>
<b>10</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>0</b>
<b>12</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>
<b>13</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>
<b>15</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>

# Quine-McCluskey Method

List 1						List 2					List 3					
mi	x1	x2	x3	x4		mi	x1	x2	x3	x4		mi	x1	x2	x3	x4
2	0	0	1	0	ok	2,6	0	-	1	0		8,9,12,13	1	-	0	-
4	0	1	0	0	ok	2,10	-	0	1	0		8,12,9,13	1	-	0	-
8	1	0	0	0	ok	4,6	0	1	-	0		Finished				
6	0	1	1	0	ok	4,12	-	1	0	0						
9	1	0	0	1	ok	8,9	1	0	0	-	ok					
10	1	0	1	0	ok	8,10	1	0	-	0						
12	1	1	0	0	ok	8,12	1	-	0	0	ok					
13	1	1	0	1	ok	9,13	1	-	0	1	ok					
15	1	1	1	1	ok	12,13	1	1	0	-	ok					
						13,15	1	1	-	1						

# Quine-McCluskey Method

List 1					List 2					List 3					
mi	x1	x2	x3	x4	mi	x1	x2	x3	x4	mi	x1	x2	x3	x4	
					2,6	0	-	1	0	8,9,12,13	1	-	0	-	t1
					2,10	-	0	1	0						
					4,6	0	1	-	0	Finished					
					4,12	-	1	0	0						
					8,10	1	0	-	0						
					13,15	1	1	-	1						

# Quine-McCluskey Method

	2	4	6	8	9	10	12	13	15
t1				X	X		X	X	
t2	X		X						
t3	X					X			
t4		X	X						
t5		X					X		
t6				X		X			
t7								X	X

	2	4	6	10
t2	X		X	
t3	X			X
t4		X	X	
t5	————— X —————			
t6	————— X —————			


t5 is a subset of t4  
t6 is a subset of t3

$$F(x_1, x_2, x_3, x_4) = t_1 + t_7 + t_3 + t_4$$

$$= x_1 x_3' + x_1 x_2 x_4 + x_2' x_3 x_4' + x_1' x_2 x_4'$$



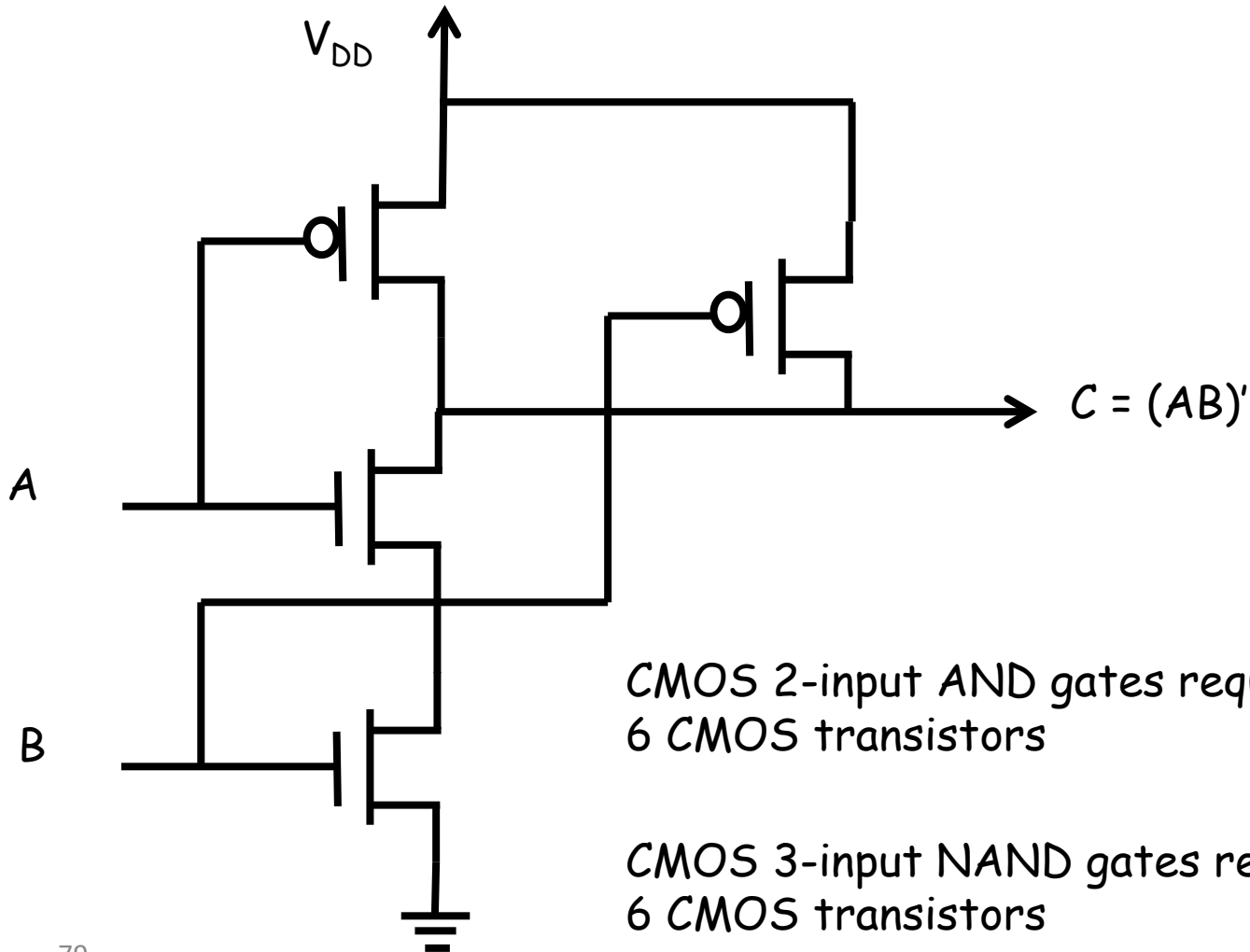
# NAND and NOR Gates

- NAND and NOR gates are easier to fabricate



   
# Design with NAND or NOR Gates

- It is beneficial to derive conversion rules from Boolean functions given in terms of AND, OR, and NOT gates into equivalent NAND or NOR implementations





# New Notation

 

- Implementing a Boolean function with NAND gates is easy if it is in sum of products form.
- Example:  $F(x, y, z, t) = xy + zt$

  
**ALWAYS USE THIS INTERMEDIATE FORM WITH BUBBLES TO AVOID CONFUSION**



$$F(x, y, z, t) = ((xy)')' + ((zt)')'$$




# The Conversion Method

 

$$((xy)')' + ((zt)')'$$

$$= xy + zt =$$

 

$$[ (xy)' (zt)' ]'$$


- Example:  $F(x, y, z) = \sum(1, 3, 4, 5, 7)$

		yz			
		00	01	11	10
x	0		1	1	
	1	1	1	1	


$$F = z + xy'$$

$$F = (z')' + ((xy)')'$$

# Example: Design with NAND Gates

 

$$F = (z')' + ((xy')')'$$

 


$$F = z + xy'$$

- **Summary**

1. Simplify the function
2. Draw a NAND gate for each product term
3. Draw a NAND gate for the OR gate in the 2<sup>nd</sup> level,
4. **A product term with single literal needs an inverter in the first level.** Assume single, complemented literals are available.

 
# Multi-Level NAND Gate Designs

- The standard form results in two-level implementations
- Non-standard forms may raise a difficulty
- Example:  $F = x(zt + y) + yz'$   
4-level implementation




# Example: Multilevel NAND...

$$F = x(zt + y) + yz'$$

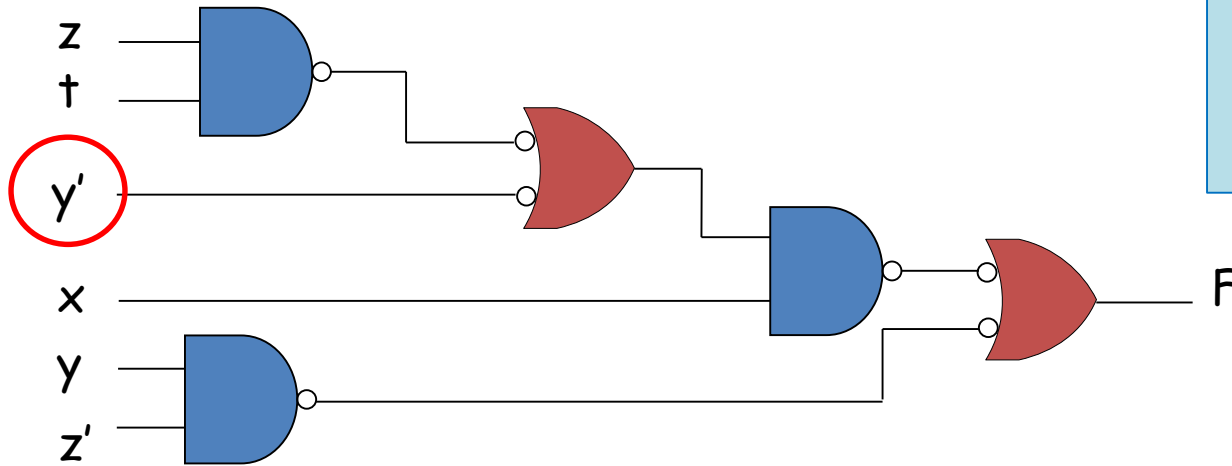

 **MUST COMPENSATE  
FOR EVERY NON-  
COUPLED BUBBLE**




# Design with Multi-Level NAND Gates

## Rules



1. Convert all AND gates to NAND gates
2. Convert all OR gates to NAND gates
- 3. Insert an inverter (one-input NAND gate) at the output if the final operation is AND**
4. Check the bubbles in the diagram. For every bubble along a path from input to output there must be another bubble. **If not so, complement the input literal**

# Another (Harder) Example

 - Example:  $F = (xy' + xy)(z + t')$   
– (three-level implementation)






# Example: Multi-Level NAND Gates

  

   
# Design with NOR Gates

- NOR is the dual operation of NAND.
  - All rules and procedure we used in the design with NAND gates apply here in a similar way.
  - Function is implemented easily if it is in product of sums form.






## Logic operations with NOR gates

 

(a) OR-invert



=

 

(b) Invert-AND



# Example: Design with NOR Gates

- $F = (x+y) (z+t) w$

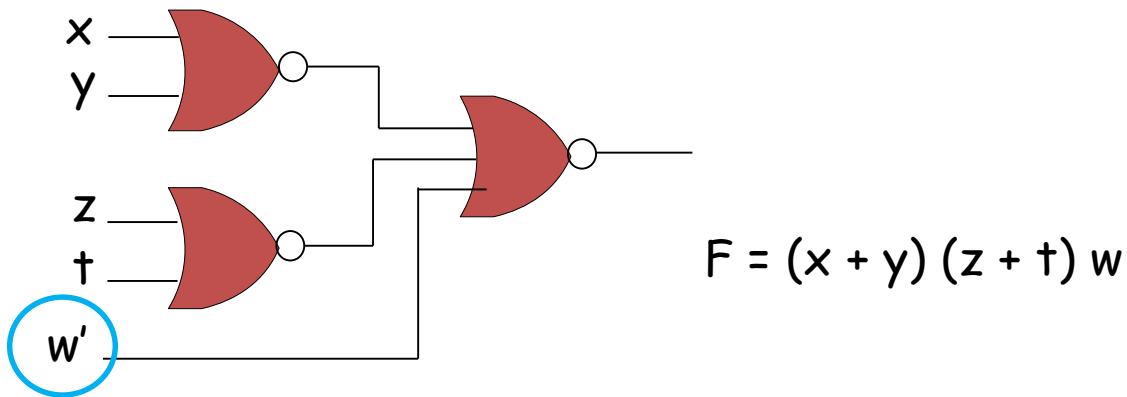 

# Example: Design with NOR Gates



- $F = (xy' + zt)(z + t')$

  

$$\begin{aligned} F &= [((x' + y)' + (z' + t'))' + (z + t)']' \\ &= ((x' + y)' + (z' + t'))(z + t) \\ &= (xy' + zt)(z + t) \end{aligned}$$

# Harder Example

- Example:  $F = x(zt + y) + yz'$

  

# Exclusive-OR Function

- The symbol:  $\oplus$

➤  $x \oplus y = xy' + x'y$

➤  $(x \oplus y)' = xy + x'y'$

- Properties

1.  $x \oplus 0 = x$

2.  $x \oplus 1 = x'$

3.  $x \oplus x = 0$

4.  $x \oplus x' = 1$

5.  $x \oplus y' = x' \oplus y = (x \oplus y)' : \text{XNOR}$

- Commutative & Associative

➤  $x \oplus y = y \oplus x$

➤  $(x \oplus y) \oplus z = x \oplus (y \oplus z)$

# Exclusive-OR Function

- XOR gate is **not** universal
  - Only a limited number of Boolean functions can be expressed in terms of XOR gates
- XOR operation has very important applications in arithmetic and error-detection circuits.
- Odd Function

$$\begin{aligned}
 (x \oplus y) \oplus z &= (xy' + x'y) \oplus z \\
 &= (xy' + x'y) z' + (xy' + x'y)' z \\
 &= xy'z' + x'yz' + (xy + x'y') z \\
 &= xy'z' + x'yz' + xyz + x'y'z \\
 &= \Sigma (4, 2, 7, 1)
 \end{aligned}$$

		yz			
	x	00	01	11	10
0		0	1	0	1
1		1	0	1	0

# Odd Function

- If an odd number of variables are equal to 1, then the function is equal to 1.
- Therefore, multivariable XOR operation is referred as “odd” function.


x \ yz	00	01	11	10
0	0	1	0	1
1	1	0	1	0

Odd function

x \ yz	00	01	11	10
0	1	0	1	0
1	0	1	0	1


Even function

# Odd & Even Functions

 

Odd function

 - $(x \oplus y \oplus z)' = ((x \oplus y) \oplus z)'$





# Adder Circuit for Integers

- Addition of two 2-bit numbers
  - $Z = X + Y$
  - $X = (x_1 x_0)$  and  $Y = (y_1 y_0)$
  - $Z = (z_2 z_1 z_0)$
- Bitwise addition
  1.  $z_0 = x_0 \oplus y_0$  (sum)  
 $c_1 = x_0 y_0$  (carry)
  2.  $z_1 = x_1 \oplus y_1 \oplus c_1$   
 $c_2 = x_1 y_1 + x_1 c_1 + y_1 c_1$
  3.  $z_2 = c_2$

# Adder Circuit


$$z_1 = x_1 \oplus y_1 \oplus c_1$$

$$c_2 = x_1 y_1 + x_1 c_1 + y_1 c_1$$

$$z_0 = x_0 \oplus y_0$$

$$c_1 = x_0 y_0$$

$$z_2 = c_2$$

 

# Comparator Circuit with NAND gates

- $F(X > Y)$

$X = (x_1 x_0)$  and  $Y = (y_1 y_0)$

$x_1 x_0 \backslash y_1 y_0$	00	01	11	10
00				
01				
11				
10				

# Comparator Circuit with NAND gates


- $F(X > Y)$

$X = (x_1 x_0)$  and  $Y = (y_1 y_0)$

$x_1 x_0 \backslash y_1 y_0$	00	01	11	10
00	0	0	0	0
01	1	0	0	0
11	1	1	0	1
10	1	1	0	0

$$F(x_1, x_0, y_1, y_0) = x_1 y_1' + x_1 x_0 y_0' + x_0 y_0' y_1'$$

# Comparator Circuit - Schematic

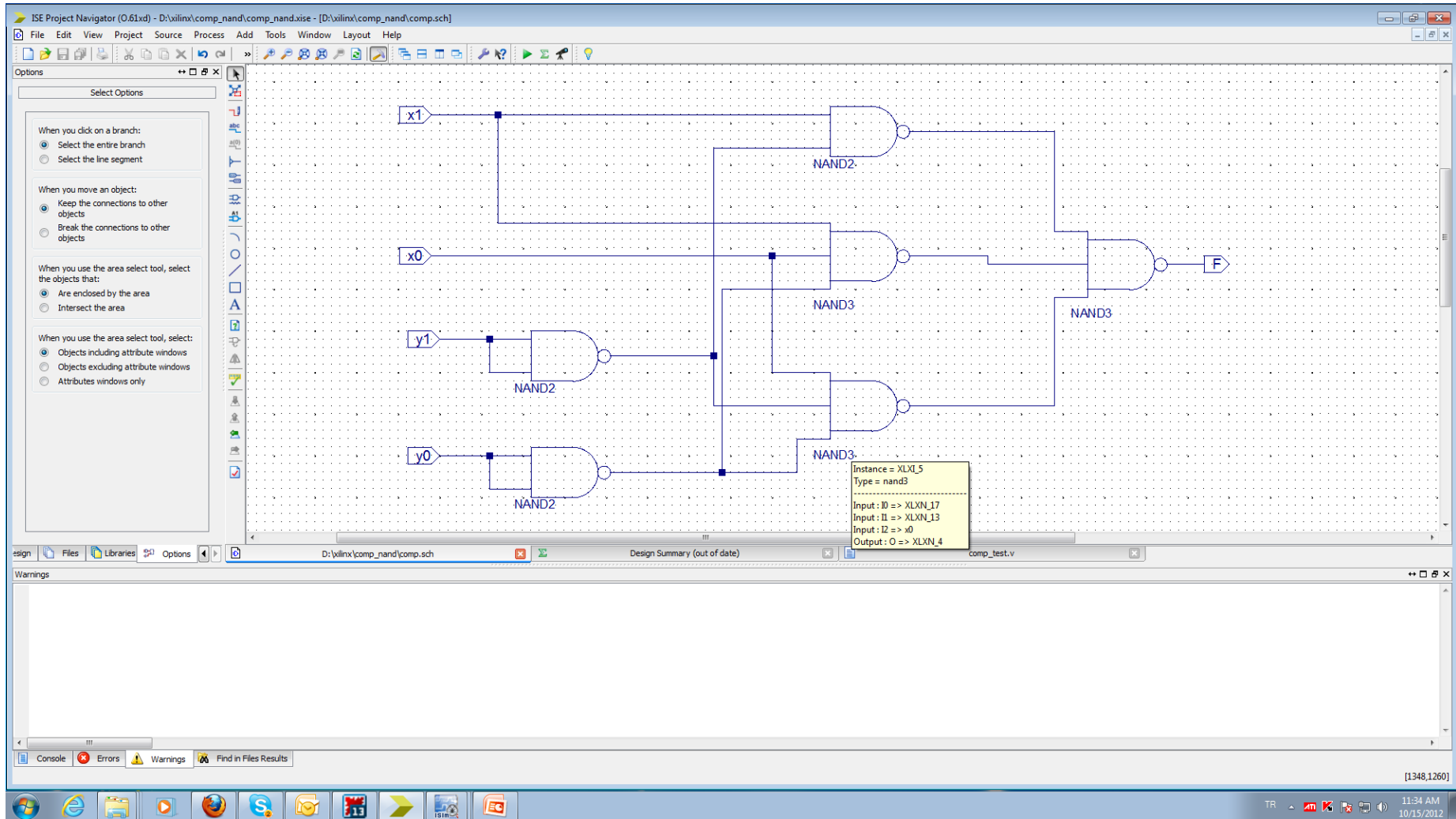

# Comparator Circuit - Simulation

