

Synchronous Sequential Logic Part I


Mantıksal Tasarım – BBM231

section instructor:
Ufuk Çelikcan

Sequential Logic

- Digital circuits we have learned, so far, have been **combinational**
 - >> no memory,
 - >> outputs are entirely defined by the “current” inputs
- However, many digital systems encountered in everyday life are **sequential** (i.e. **they have memory**)
 - the memory elements remember past inputs
 - outputs of sequential circuits are not only dependent on the current input but also the state of the memory elements.

Sequential Circuits Model

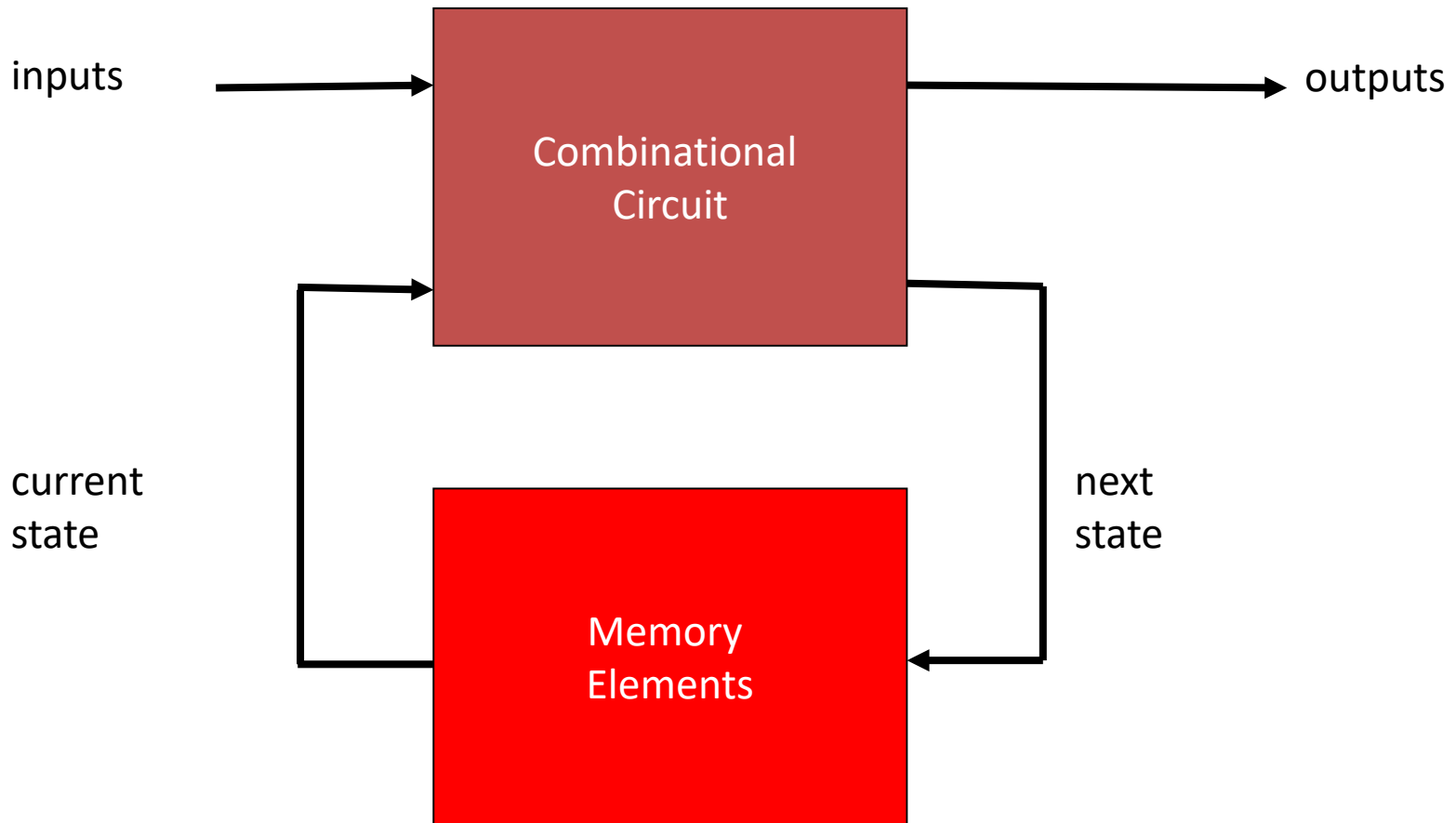

current state is a function of **past inputs + initial state**

Classification

There are 2 types of sequential circuits

1. Synchronous

- Signals affect the memory elements at discrete instants of time.
- Discrete instants of time requires synchronization.
- Synchronization is usually achieved through the use of a common clock.
- A “clock generator” is a device that generates a periodic train of pulses.



Classification

1. Synchronous


- The state of the memory elements are updated with the arrival of each pulse
- This type of logical circuit is also known as clocked sequential circuits.

2. Asynchronous

- No clock
- Behavior of an asynchronous sequential circuit depends upon the input signals at any instant of time and the order in which the inputs change.
- Memory elements in asynchronous circuits are regarded as time-delay elements

Clocked Sequential Circuits

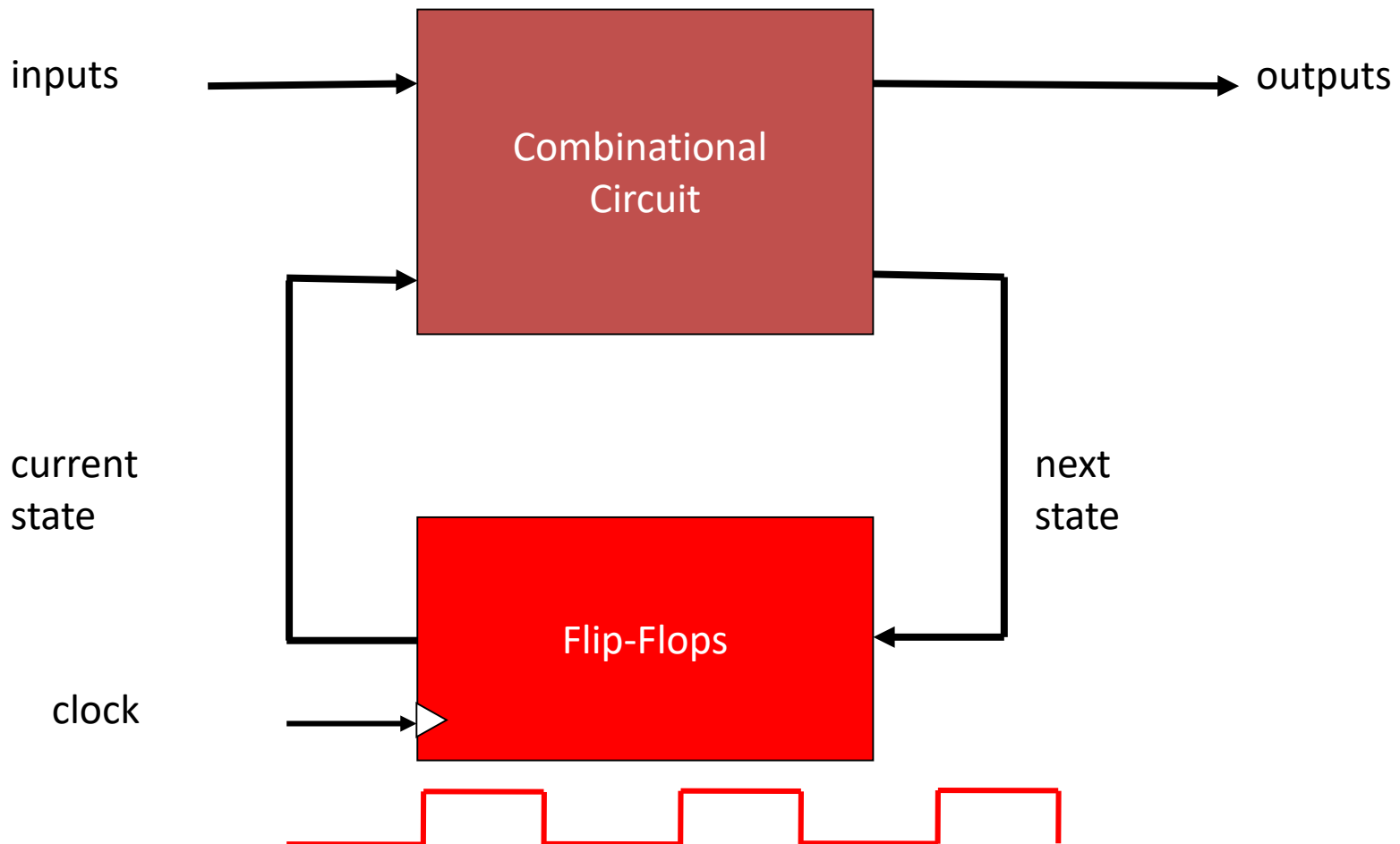- Memory elements are flip-flops which are logic devices, each of which is capable of storing one bit of information.



Clocked Sequential Circuits

- The outputs of a clocked sequential circuit can come from
 - the combinational circuit,
 - the outputs of the flip-flops
 - or both.
- The state of the flip-flops can change only during a clock pulse transition
 - i.e. **low-to-high** and **high-to-low**
 - **clock edge**
- When the clock maintains its value, the flip-flop output does not change
- The transition from one state to the next occurs at the clock edge.

Machine

Machine (

Inputs $\{X\}$,

States $\{D\}$,

Outputs $\{Z\}$,

Output Function $\{F : X \times D \rightarrow Z\}$,


Next State Function $\{G : X \times D \rightarrow D\}$

)

Representation with State Diagram


	x_1	x_2	\dots	x_i	\dots	x_l
d_1						
d_2						
\vdots						
d_i				$d_{j,z}$		
\vdots						
d_{r-1}						
d_r						

Assign a Node to Each State

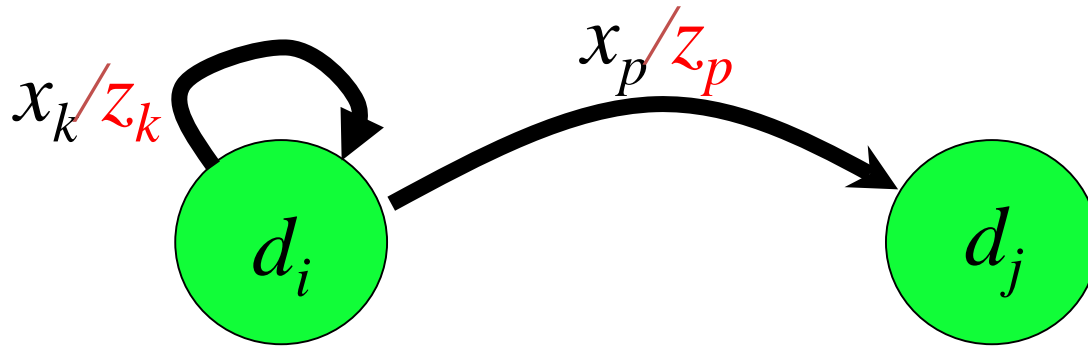

- Machine is at state d_i , input x_k comes, the next state will be again d_i and the output is z_k
- Machine is at state d_i , input x_p comes, the next state will be d_j and the output is z_p

Assign a Node to Each State

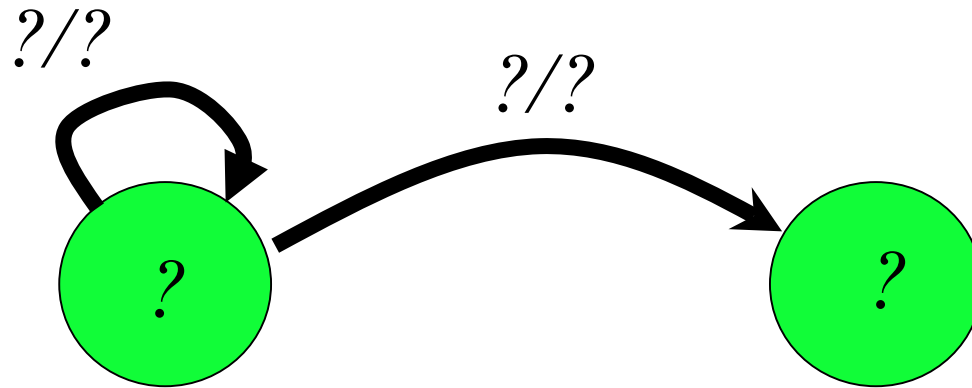

- Machine is at state d_m , input x_t comes, the next state will be again d_m and the output is z_t
- Machine is at state d_m , input x_u comes, the next state will be d_n and the output is z_u


Notation

- Let I_k be an **input sequence** with length equal to k , i.e. $I_k = x_1x_2\dots x_k$
- $f(I_k, d_i) = z_1z_2\dots z_k$ is an **output sequence**
- $g(I_k, d_i) = d_{i1}d_{i2}\dots d_{ik}$ is a **state sequence**
- $d_i \xrightarrow{I_k} d_{ik}$: **Follower** of d_i after the input sequence I_k

Example - Fill out the rest



	0	1
A	E, 0	D, 1
B	F, 0	D, 0
C	E, 0	B, 1
D	F, 0	B, 0
E	C, 0	F, 1
F	B, 0	C, 0

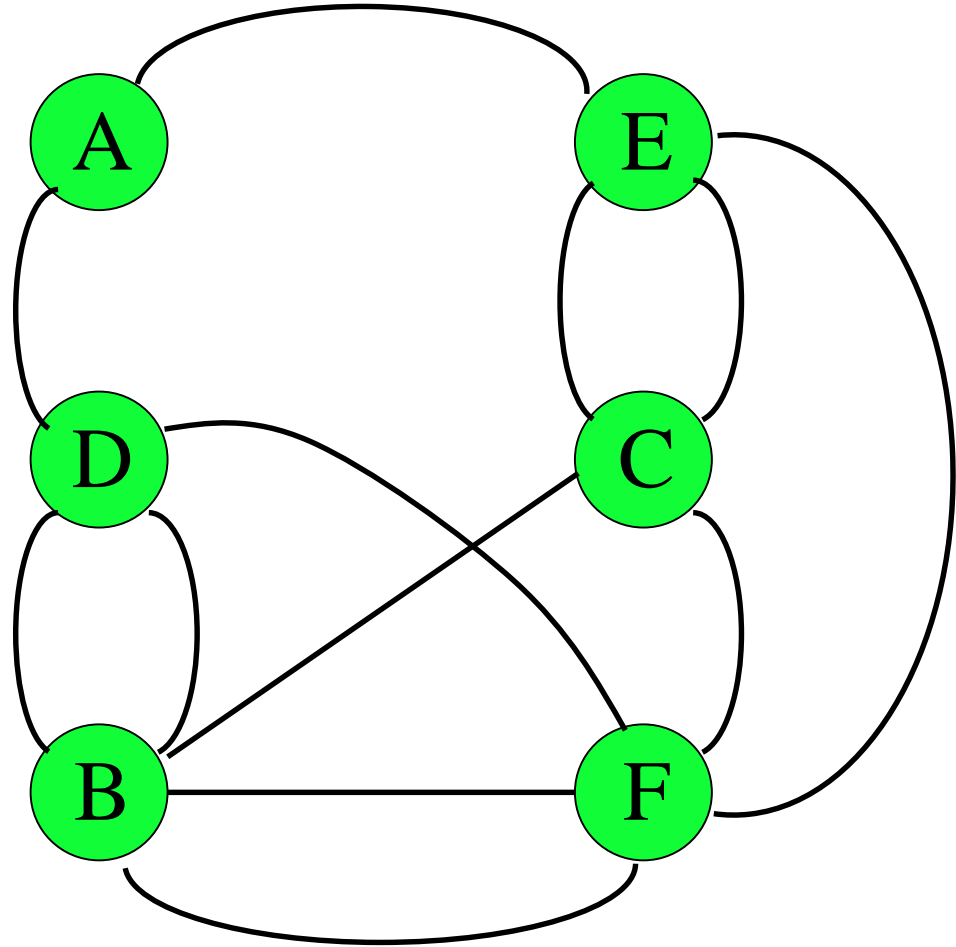

Example

	0	1
A	E, 0	D, 1
B	F, 0	D, 0
C	E, 0	B, 1
D	F, 0	B, 0
E	C, 0	F, 1
F	B, 0	C, 0

- Let $l_5=10110$, find $g(l_5, C)$ and $f(l_5, C)$

l_5						
$g(l_5, C)$						
$f(l_5, C)$						

- l_5 follower of C : ?

Example


	0	1
A	E, 0	D, 1
B	F, 0	D, 0
C	E, 0	B, 1
D	F, 0	B, 0
E	C, 0	F, 1
F	B, 0	C, 0

- Let $l_5=10110$, find $g(l_5, C)$ and $f(l_5, C)$

l_5		1	0	1	1	0
$g(l_5, C)$	C	B	F	C	B	F
$f(l_5, C)$		1	0	0	1	0

- l_5 follower of C is F

D Flip-Flop

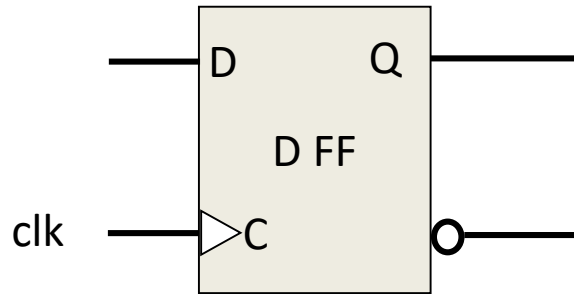

Positive edge-triggered
D Flip-Flop


- **Characteristic equation**

$$Q(t+1) = D$$

D	Q(t+1)
0	0
1	1

Characteristic Table


Timing Diagram of D Flip-Flop

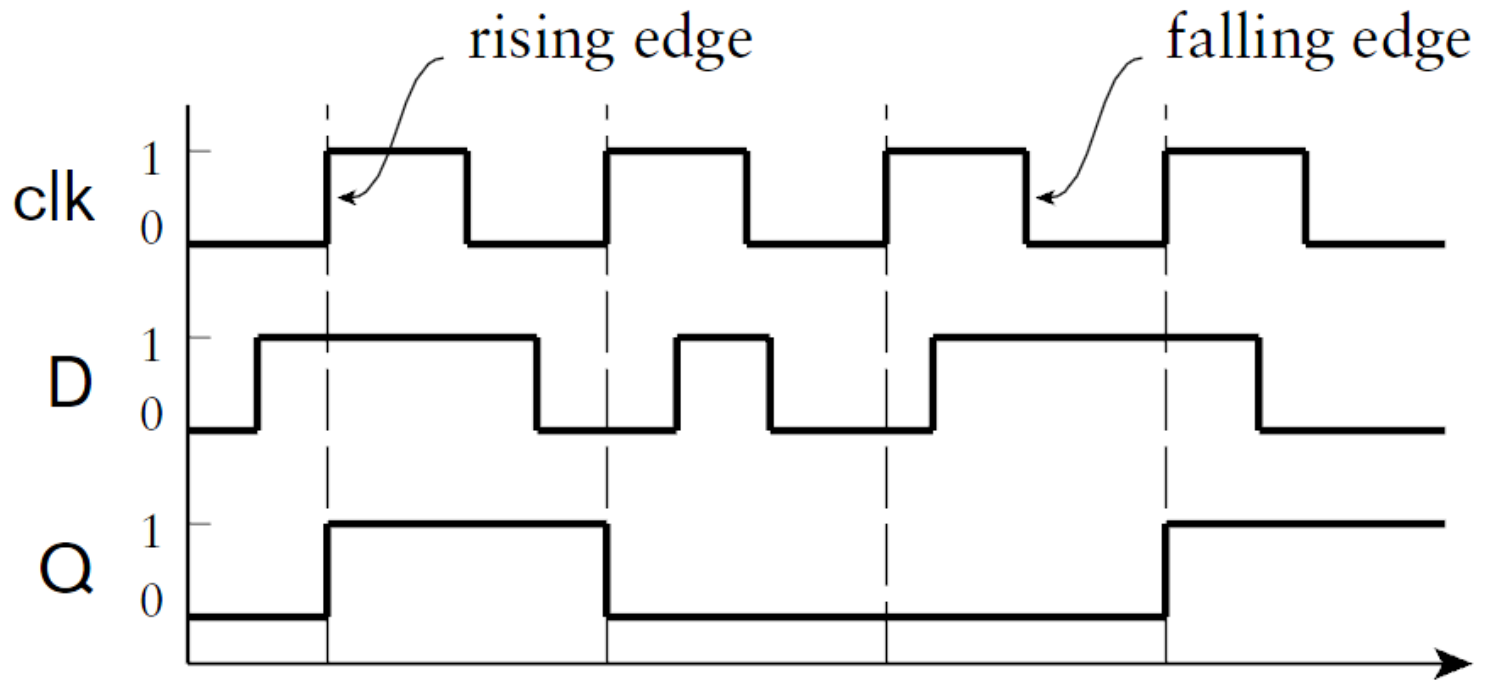

Other Flip-Flops

- D flip-flop is the most common
 - since it requires the fewest number of gates to construct.
- Two other widely used flip-flops
 - JK flip-flops
 - T flip-flops
- JK flip-flops
 - Three FF operations
 1. Set
 2. Reset
 3. Complement

JK Flip-Flops

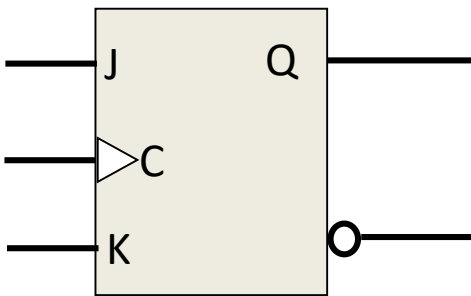


J	K	Q(t+1)	next state
0	0	Q(t)	no change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

Characteristic Table

Characteristic Equation of JK flip-flop?

JK Flip-Flops

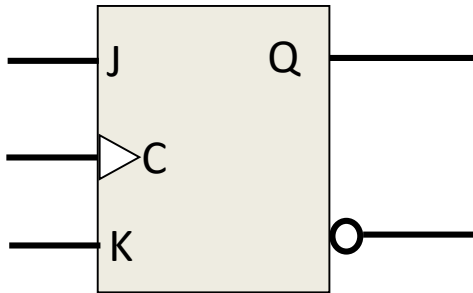


J	K	Q(t+1)	next state
0	0	Q(t)	no change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

Characteristic Table

J	K	Q(t)	Q(t+1)
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

JK Flip-Flops

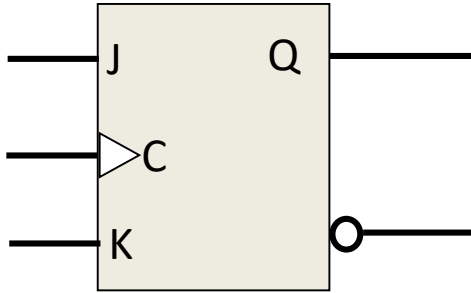

J	K	Q(t+1)	next state
0	0	Q(t)	no change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement


J	K	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Characteristic Table

K, Q(t)		J			
		00	01	11	10
J	0	0	1	0	0
	1	1	1	0	1

Q(t+1) = ?


JK Flip-Flops

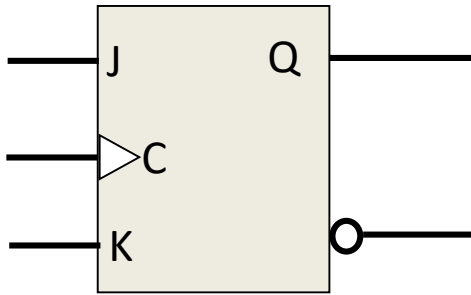

J	K	Q(t+1)	next state
0	0	Q(t)	no change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement


J	K	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Characteristic Table

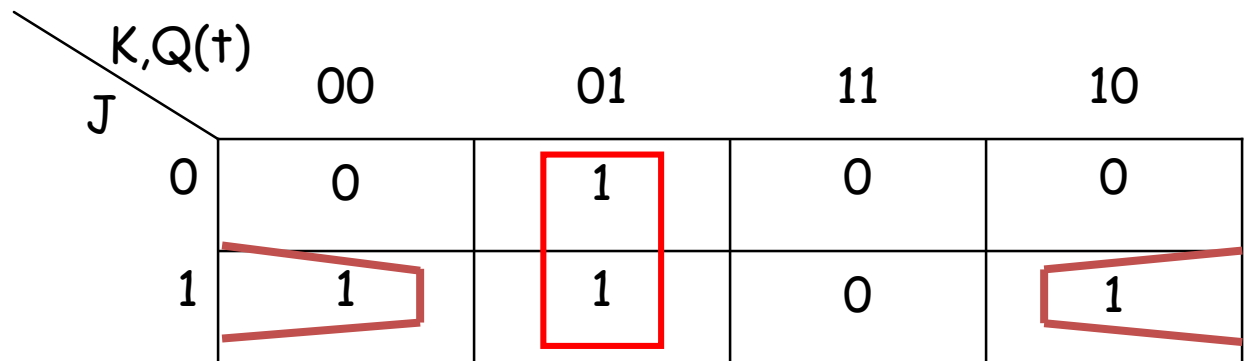

Q(t+1) = ?

JK Flip-Flops

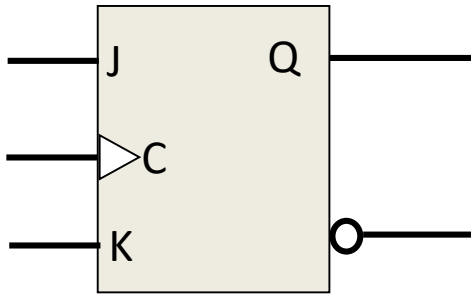


J	K	Q(t+1)	next state
0	0	Q(t)	no change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

Characteristic Table

- Characteristic equation
$$Q(t+1) = JQ'(t) + K'Q(t)$$

T (Toggle) Flip-Flop

- Complementing flip-flop


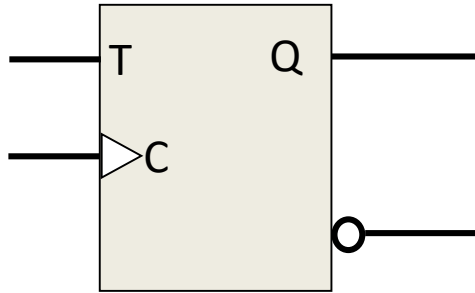


T	Q(t+1)	next state
0	Q(t)	no change
1	Q'(t)	Complement

Characteristic Table


- Characteristic equation

$$Q(t+1) = ?$$

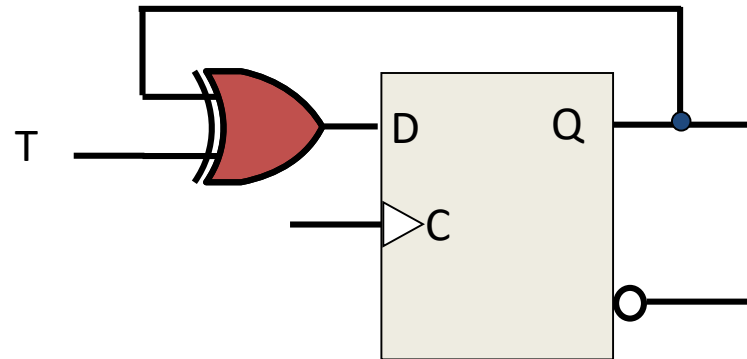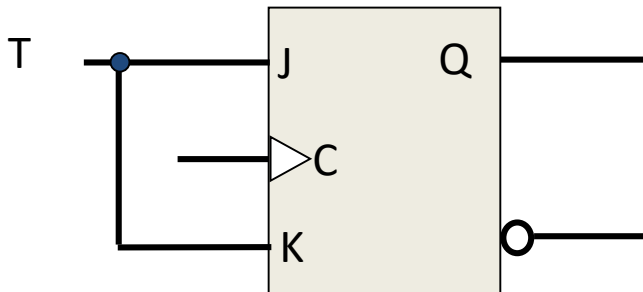

T (Toggle) Flip-Flop

- Complementing flip-flop


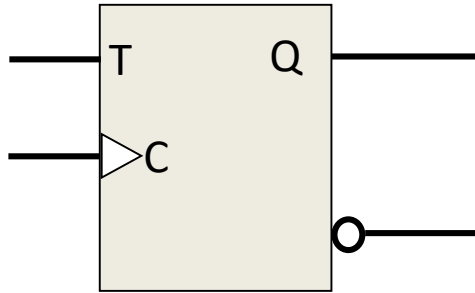


T	Q(t+1)	next state
0	Q(t)	no change
1	Q'(t)	Complement

Characteristic Table

- Characteristic equation

$$Q(t+1) = Q(t) \oplus T$$

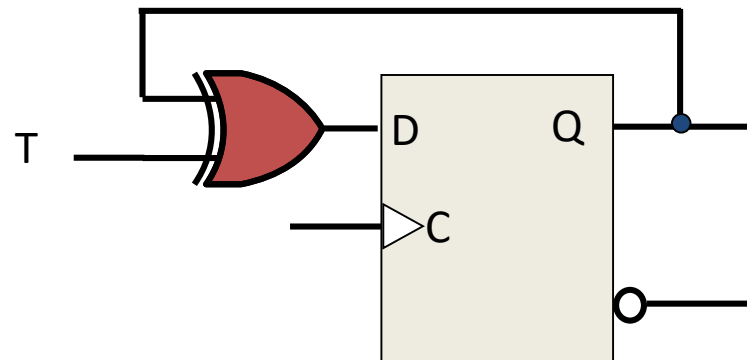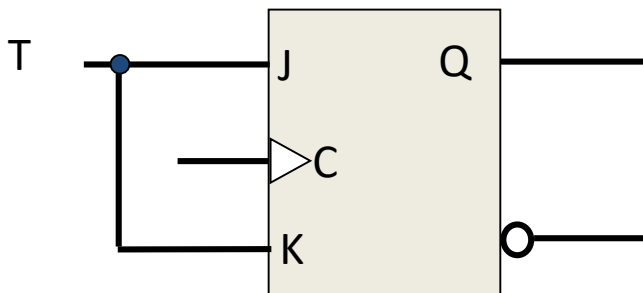

Characteristic Equations

The logical properties of a flip-flop can be expressed algebraically using characteristic equations :

- D flip-flop

$$Q(t+1) = D$$

- JK flip-flop

$$Q(t+1) = JQ'(t) + K'Q(t)$$

- T flip-flop

$$Q(t+1) = Q(t) \oplus T$$

What if we have $Q(t+1)$ and $Q(t)$, and looking for J and K values?

$Q(t)Q(t+1)$	00	01	11	10
J,K	0,X	1,X	X,0	X,1

$$J = \begin{cases} Q(t+1) & Q(t)=0 \\ X & Q(t)=1 \end{cases}$$

$$K = \begin{cases} Q(t+1)' & Q(t)=1 \\ X & Q(t)=0 \end{cases}$$

What if we have $Q(t+1)$ and $Q(t)$, and looking for D value?

$Q(t)Q(t+1)$	00	01	11	10
D	0	1	1	0

$D = Q(t+1)$

What if we have $Q(t+1)$ and $Q(t)$, and looking for T value?


$Q(t)Q(t+1)$	00	01	11	10
T	0	1	0	1

$$T = Q(t) \oplus Q(t+1)$$

Asynchronous Inputs of Flip-Flops

- They are used to force the flip-flop to a particular state independent of clock
 - “Preset” (direct set) set FF state to 1
 - “Clear” (direct reset) set FF state to 0
- They are especially useful at startup.
 - In digital circuits when the power is turned on, the state of flip-flops are unknown.
 - Asynchronous inputs are used to bring all flip-flops to a known “starting” state prior to clock operation.

Asynchronous Inputs

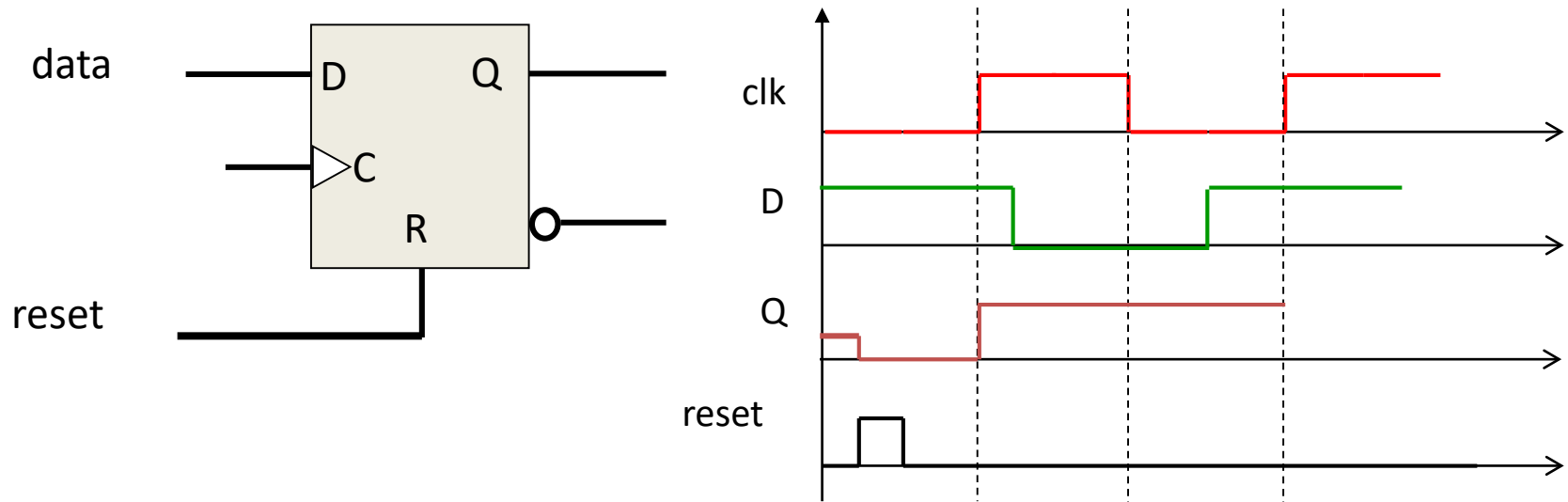


<i>reset</i>	<i>C</i>	<i>D</i>	<i>Q</i>	<i>Q'</i>	
1	X	X	0	1	Starting State
0	↑	0	0	1	
0	↑	1	1	0	


Analysis of Clocked Sequential Circuits



- Goal:
 - to determine the **behavior** of clocked sequential circuits
 - “Behavior” is determined from
 - Inputs
 - Outputs
 - State of the flip-flops
 - We have to obtain
 - Boolean expressions for output and next state
 - output & state equations
 - (state) table
 - (state) diagram

Analyze the circuit

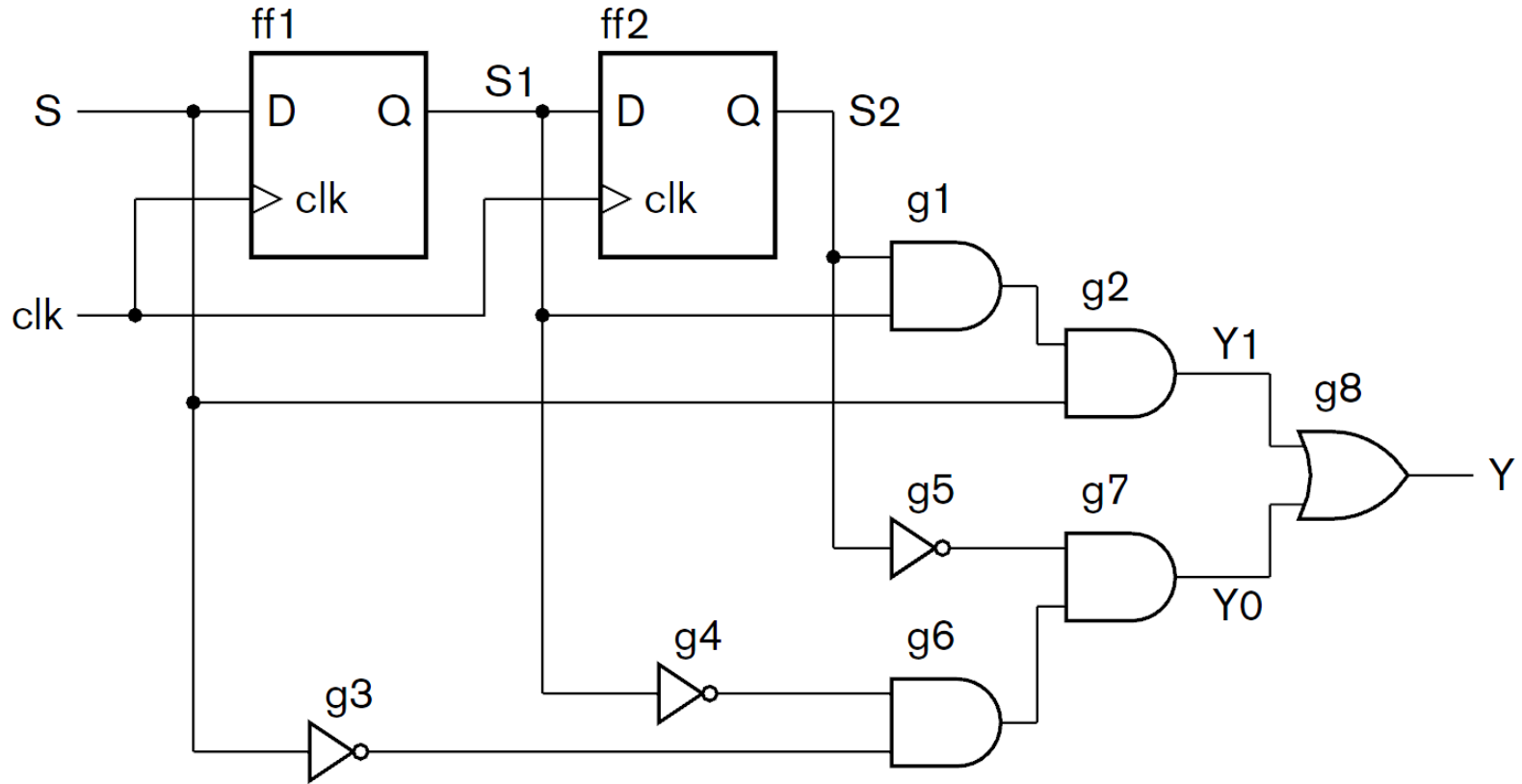

Run it and check the timing diagram

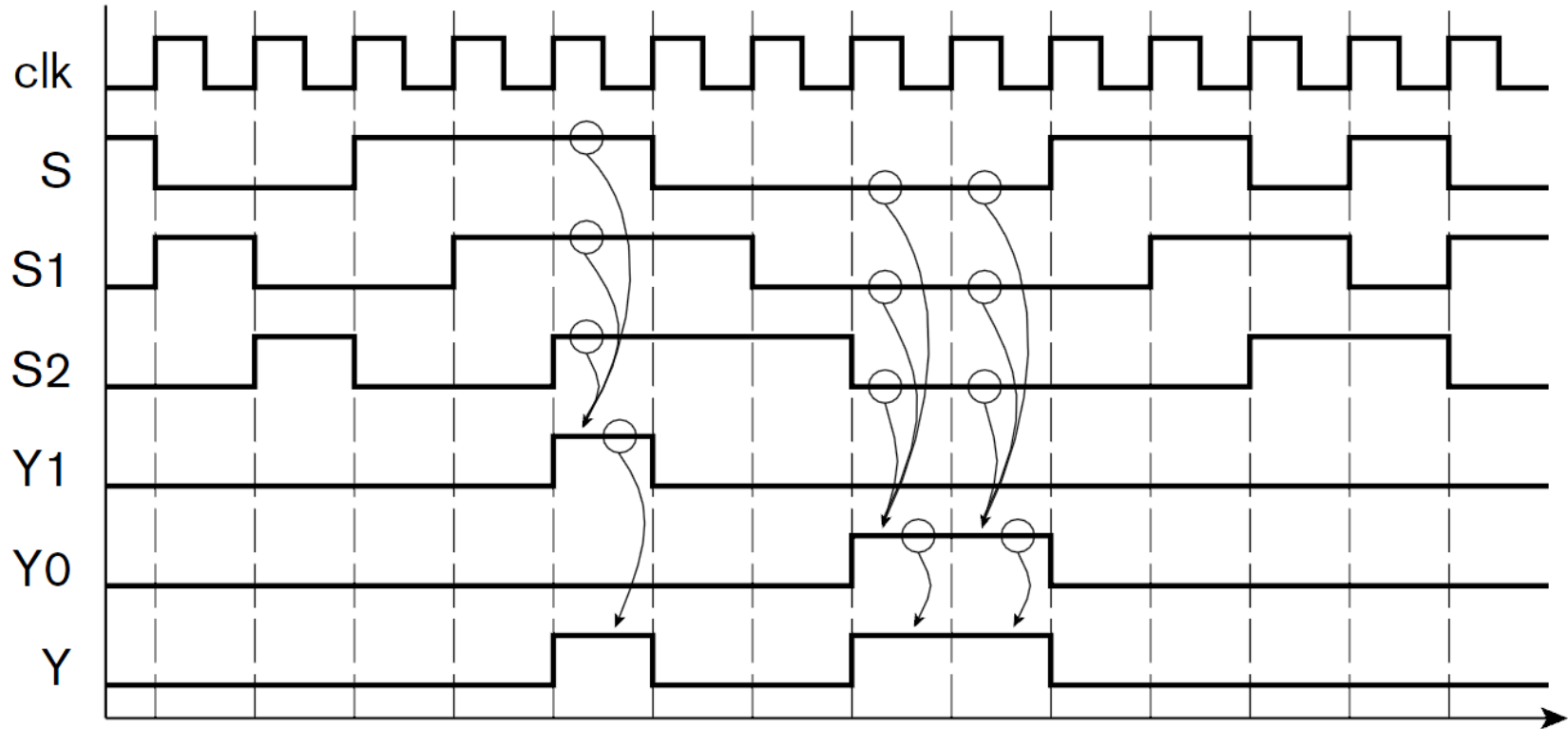


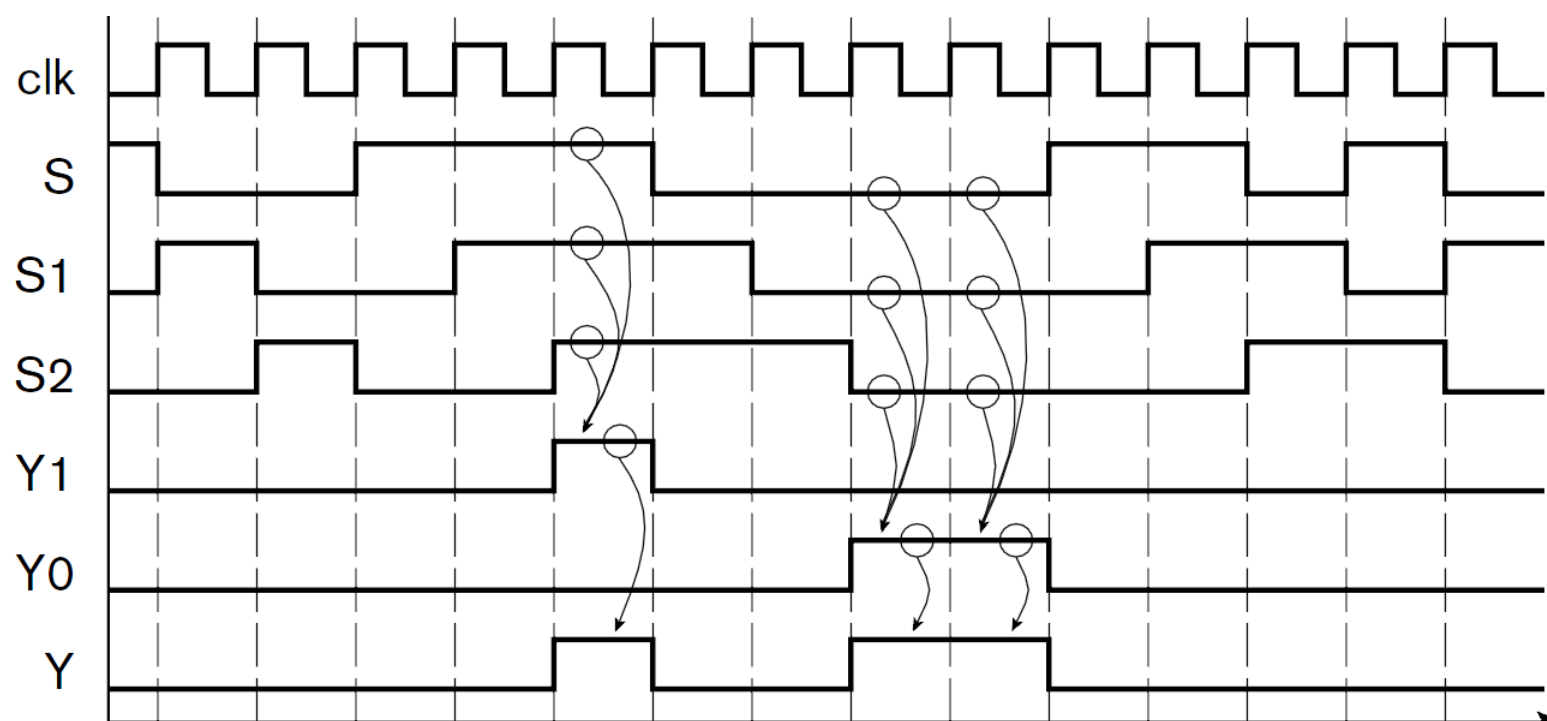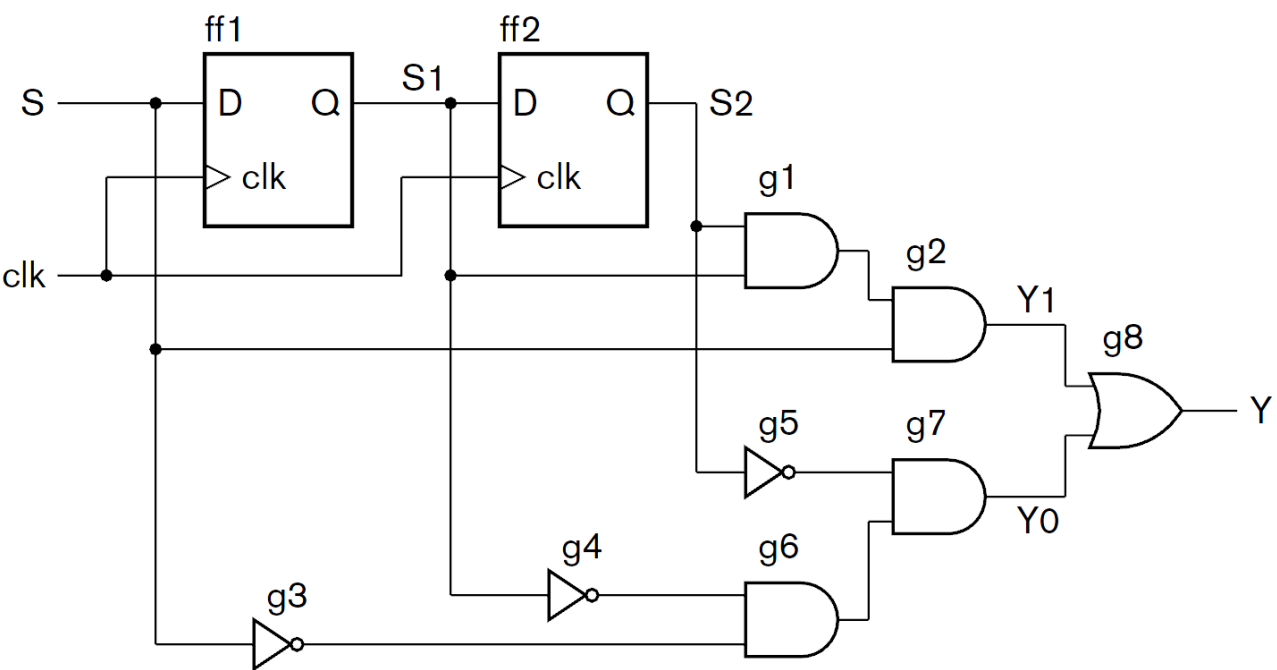

State Equations

- Also known as “transition equations”
 - specify the next state as a function of the present state and inputs


- Example

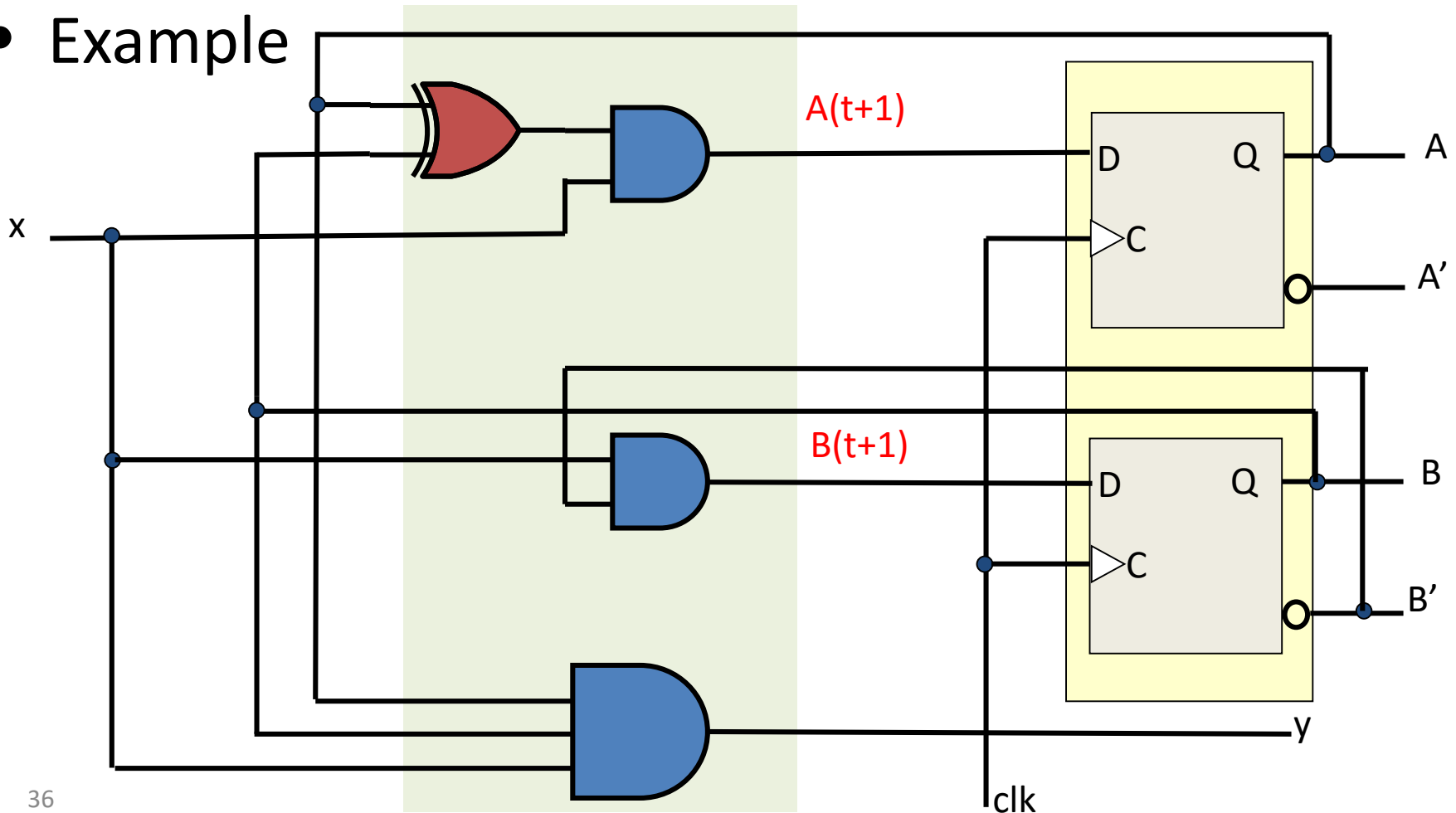

Output and State Equations


- $A(t+1) =$
- $B(t+1) =$
- $y =$

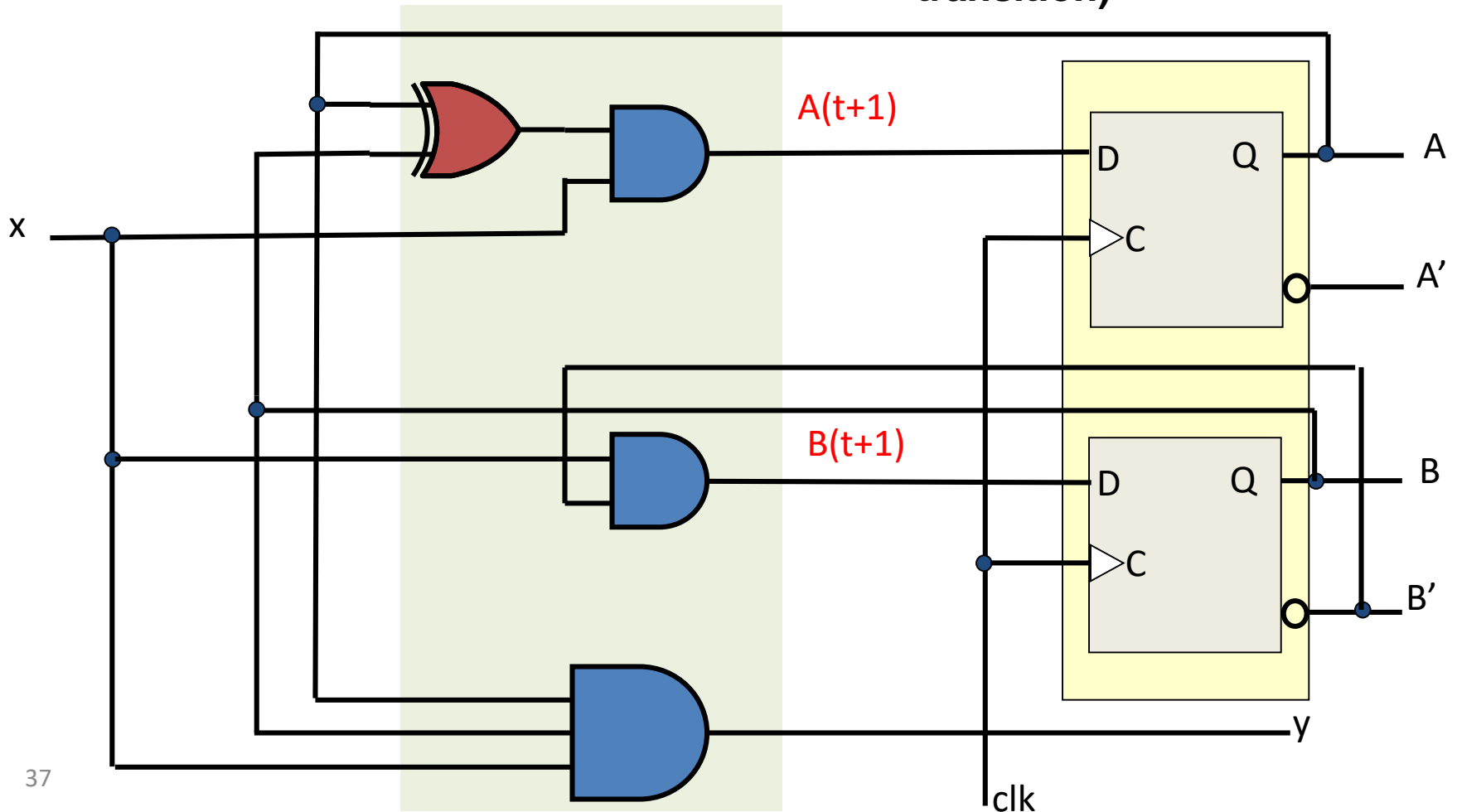input of a flip-flop determines the value of the next state (i.e., the state reached after the clock transition)



Output and State Equations

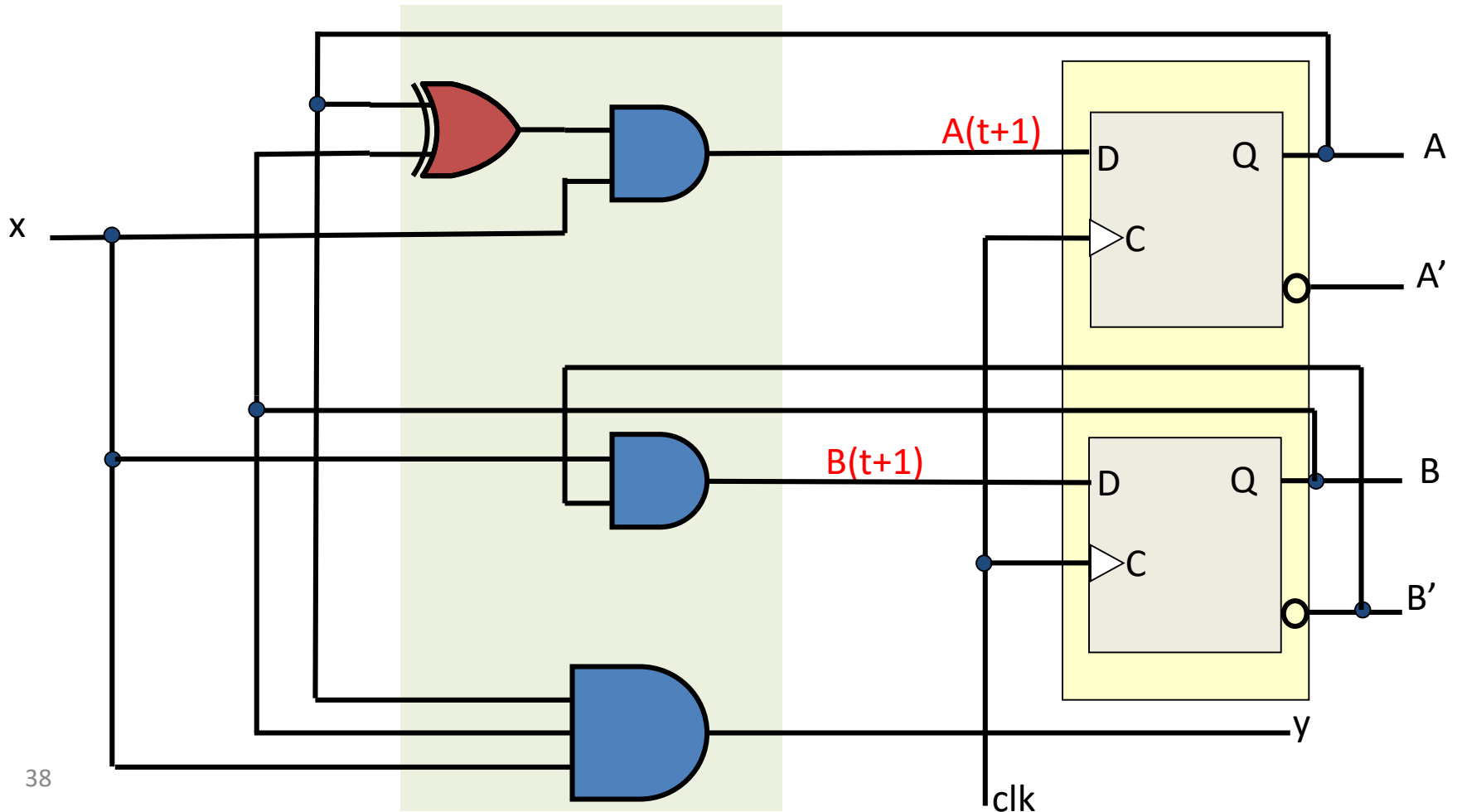- $A(t+1) = (A(t) \oplus B(t)) x$
- $B(t+1) = (B(t))' x$
- $y = A(t)B(t) x$



Flip Flop Input Equations

- Flip-Flop input (excitation) equations
- Same as the state equations in D flip-flops

Example: State (Transition) Table

$$A(t+1) = (AB' + A'B)x$$

$$B(t+1) = B'x$$

$$Y = ABx$$

Present state		input	Next state		output
A(t)	B(t)	x	A(t+1)	B(t+1)	y
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

A sequential circuit with **m** FFs and **n** inputs needs 2^{m+n} rows in the transition table

Example: State (Transition) Table

$$A(t+1) = (AB' + A'B)x$$


$$B(t+1) = B'x$$

$$Y = ABx$$

Present state		input x	Next state		output y
A(t)	B(t)		A(t+1)	B(t+1)	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	0	0	1

A sequential circuit with **m** FFs and **n** inputs needs 2^{m+n} rows in the transition table

Example: State Diagram

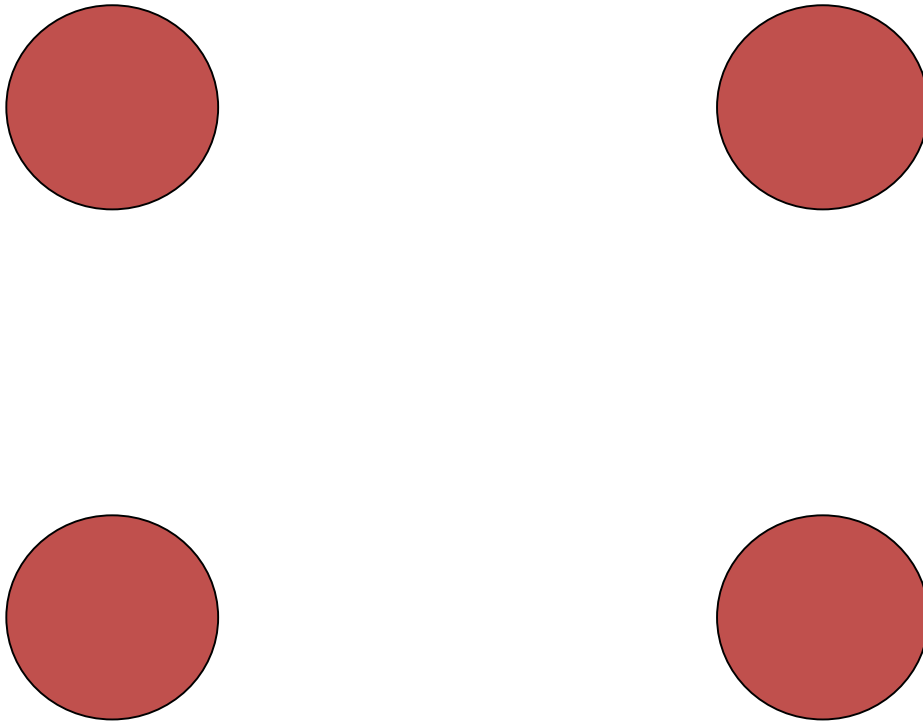


Present state		input x	Next state		output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	0	0	1

What is this circuit doing?

State diagram provides the same information as state table

Example: State Diagram

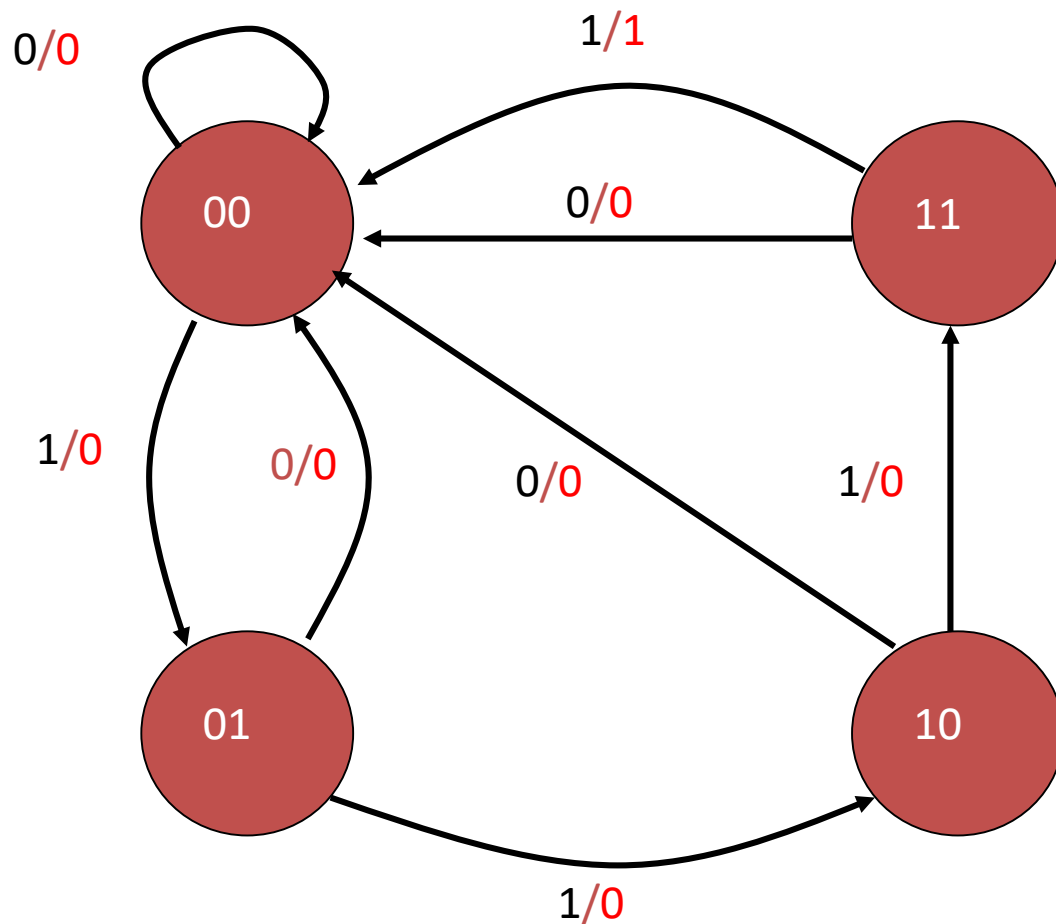

Present state		input	Next state		output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	0	0	1


What is this circuit doing?

State diagram provides the same information as state table

Analysis with JK Flip-Flops

- For a D flip-flop, the state equation is the same as the flip-flop input equation
 - $Q(t+1) = D$
- For JK flip-flops, situation is different
 - Goal is to find state equations
 - Method
 1. Determine flip-flop input equations
 2. List the binary values of each input equation
 3. Use the corresponding flip-flop characteristic table to determine the next state values in the state table

Example: Analysis with JK FFs

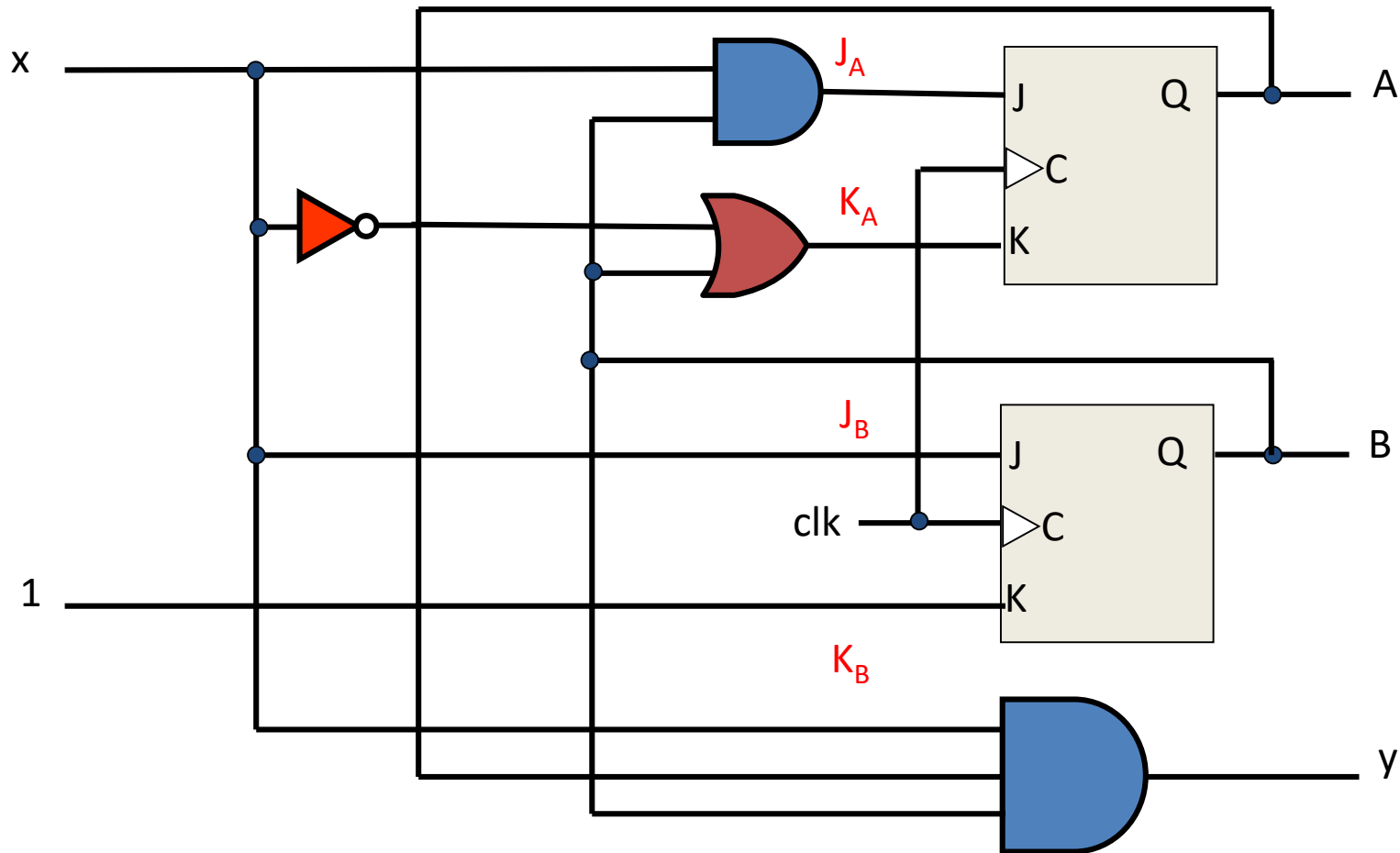

- Flip-flop input equations

$$J_A = \quad \text{and } K_A =$$

$$J_B = \quad \text{and } K_B =$$

Example: Analysis with JK FFs

- $J_A = Bx$ and $K_A = x'+B$
- $J_B = x$ and $K_B = 1$

present State		input	next state		FF inputs			
A(t)	B(t)	x	A(t+1)	B(t+1)	J_A	K_A	J_B	K_B
0	0	0						
0	0	1						
0	1	0						
0	1	1						
1	0	0						
1	0	1						
1	1	0						
1	1	1						

Example: Analysis with JK FFs

- $J_A = Bx$ and $K_A = x'+B$
- $J_B = x$ and $K_B = 1$

Characteristic equations

- $A(t+1) = ?$
- $B(t+1) = ?$
- $y = ?$

present State		input	next state		FF inputs			
A(t)	B(t)	x	A(t+1)	B(t+1)	J_A	K_A	J_B	K_B
0	0	0	0	0	0	1	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	0	0	1	0	1
0	1	1	1	0	1	1	1	1
1	0	0	0	0	0	1	0	1
1	0	1	1	1	0	0	1	1
1	1	0	0	0	0	1	0	1
1	1	1	0	0	1	1	1	1





Example: Analysis with JK FFs

- Characteristic equations
 - $A(t+1) = J_A A' + K'_A A$
 - $B(t+1) = J_B B' + K'_B B$
 - $y = ABx$
- Input equations
 - $J_A = Bx$ and $K_A = x' + B$
 - $J_B = x$ and $K_B = 1$
- State equations
 - $A(t+1) =$
 $=$
 - $B(t+1) =$

Example: Analysis with JK FFs

- Characteristic equations
 - $A(t+1) = J_A A' + K'_A A$
 - $B(t+1) = J_B B' + K'_B B$
 - $y = ABx$
- Input equations
 - $J_A = Bx$ and $K_A = x' + B$
 - $J_B = x$ and $K_B = 1$
- State equations
 - $A(t+1) = A'Bx + (x' + B)' A$
 $= A'Bx + AB'x = (A \oplus B) x$
 - $B(t+1) = B'x$


State Diagram

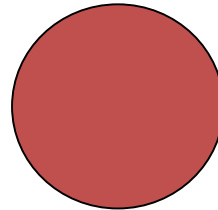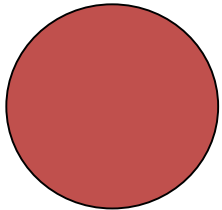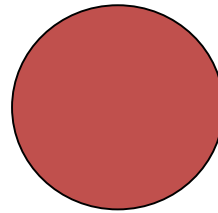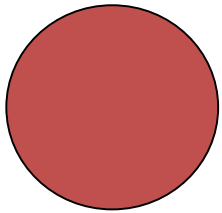

Present state		input	Next state		output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	0	0	1

What is the circuit doing?

State Diagram

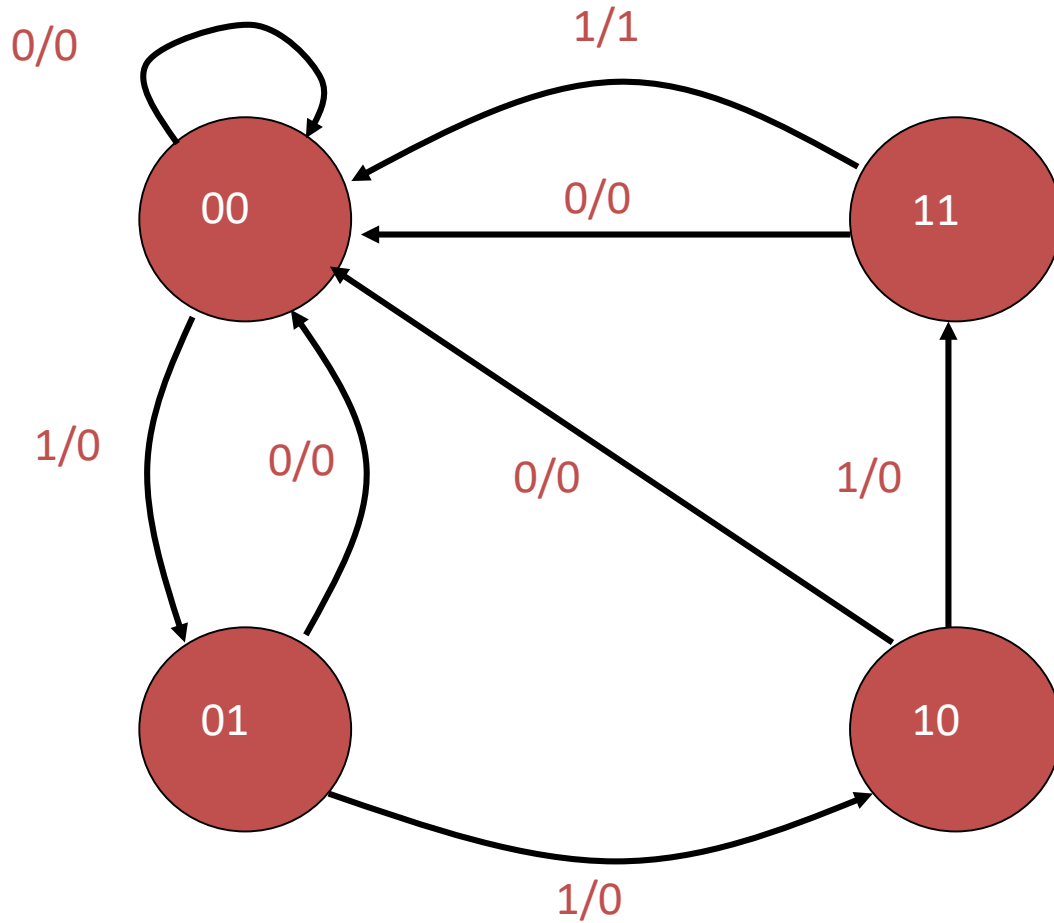

Present state		input	Next state		output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	0	0	1


What is the circuit doing?

Analysis with T Flip-Flops

- Method is the same
- Example

$$T_A =$$

$$T_B =$$

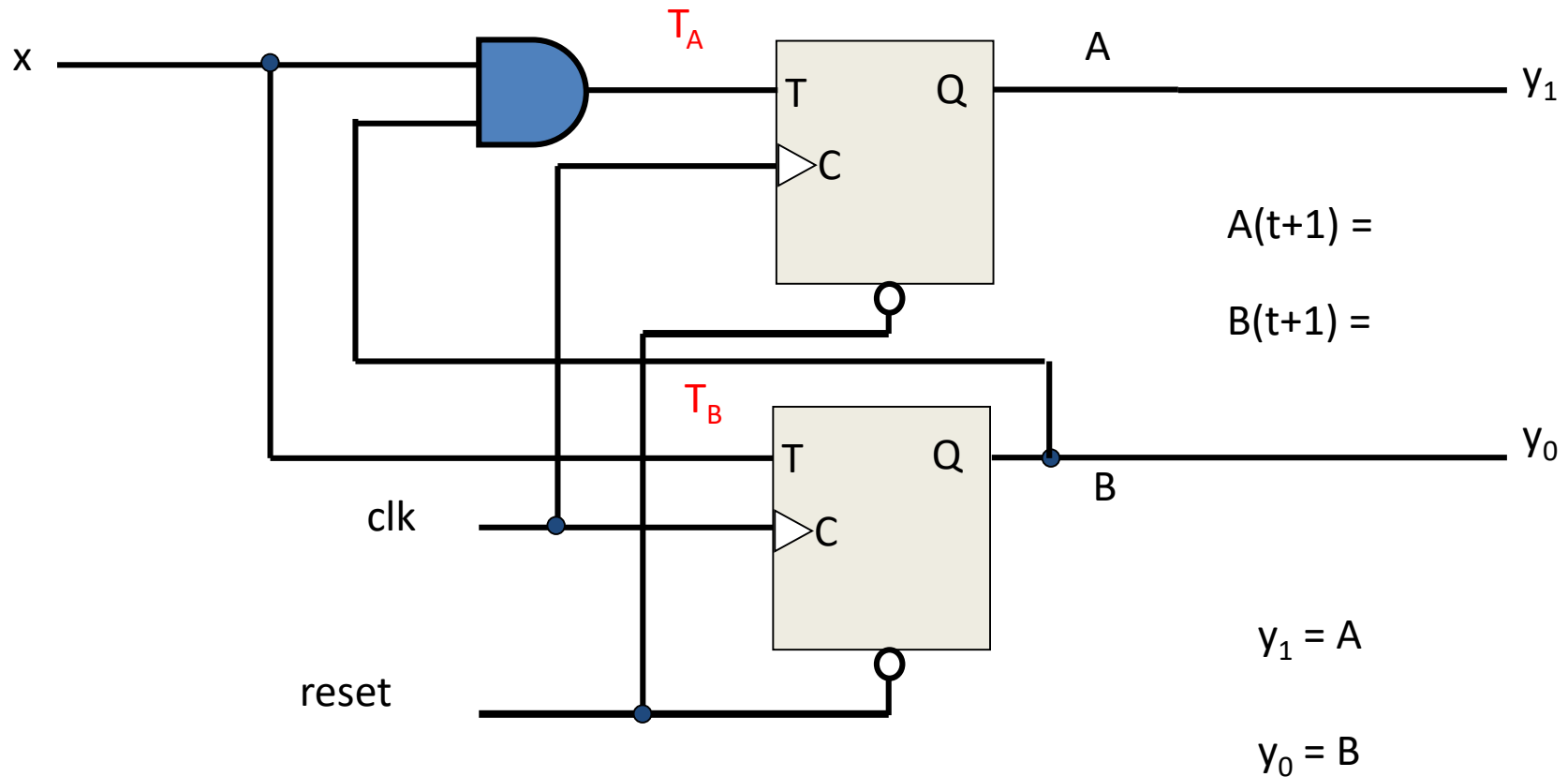





Example: Analysis with T Flip-Flops

- Characteristic equation
 - $A(t+1) = T_A \oplus A$
 - $B(t+1) = T_B \oplus B$
- Input equations
 - $T_A = Bx$
 - $T_B = x$
- Output equations
 - $y_1 = A$
 - $y_0 = B$
- State equations
 - $A(t+1) =$
 - $B(t+1) =$

State Table & Diagram

- $A(t+1) = xB \oplus A$
- $B(t+1) = x \oplus B$
- $y_1 = A; y_0 = B$





Present state		input x	Next state		output	
A	B		A	B	y_1	y_0
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

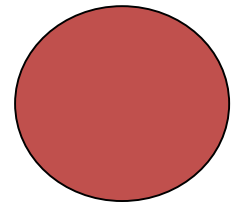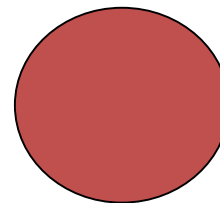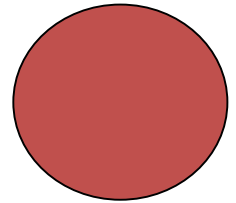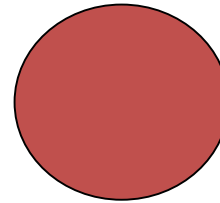

State Table & Diagram

- $A(t+1) = xB \oplus A$
- $B(t+1) = x \oplus B$
- $y_1 = A; y_0 = B$


Present state		input x	Next state		output	
A	B		A	B	y_1	y_0
0	0	0	0	0	0	0
0	0	1	0	1	0	0
0	1	0	0	1	0	1
0	1	1	1	0	0	1
1	0	0	1	0	1	0
1	0	1	1	1	1	0
1	1	0	1	1	1	1
1	1	1	0	0	1	1

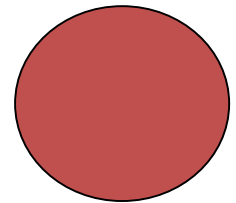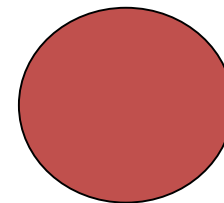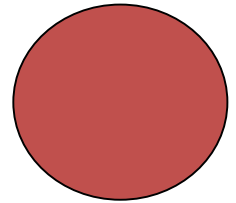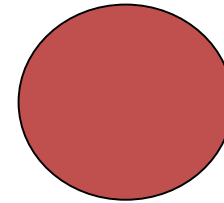

State Table & Diagram

- $A(t+1) = xB \oplus A$
- $B(t+1) = x \oplus B$
- $y_1 = A; y_0 = B$


Present state		input	Next state		output	
A	B		A	B	y_1	y_0
0	0	0	0	0	0	0
0	0	1	0	1	0	0
0	1	0	0	1	0	1
0	1	1	1	0	0	1
1	0	0	1	0	1	0
1	0	1	1	1	1	0
1	1	0	1	1	1	1
1	1	1	0	0	1	1

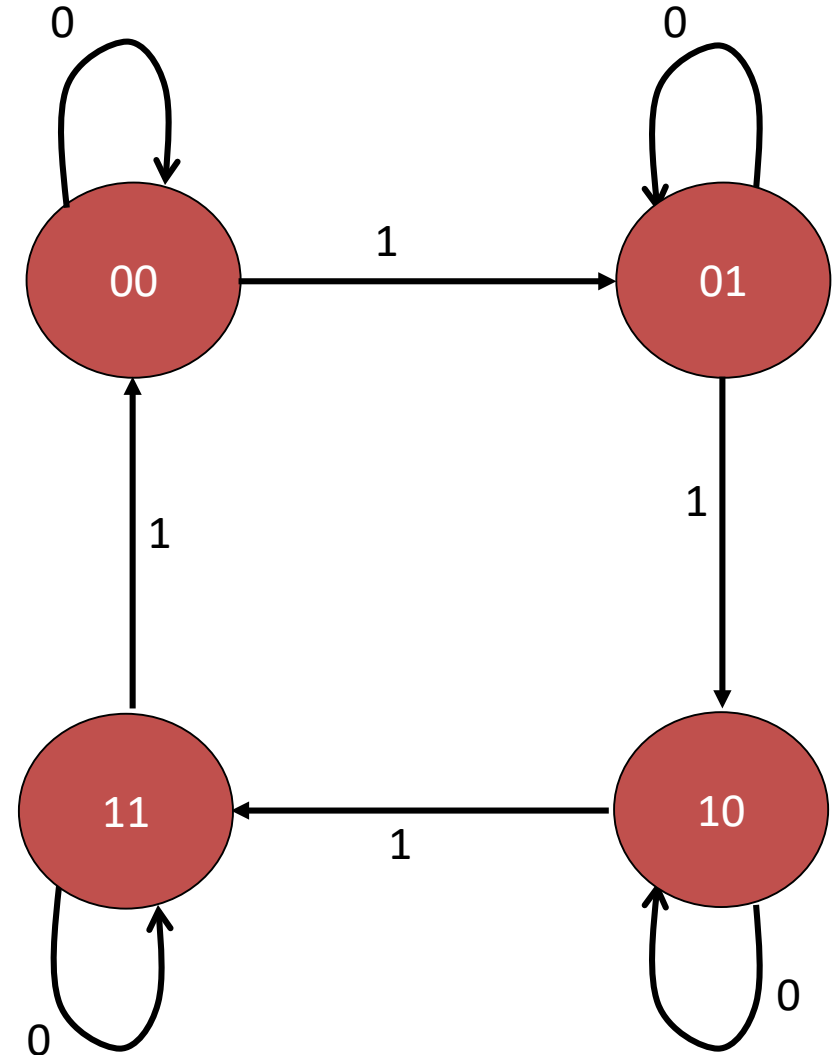

Mealy and Moore Models

- There are two models for sequential circuits
 - Mealy
 - Moore
- They differ in the way the outputs are generated
 - Mealy:
 - output is a function of **both present states and inputs**
 - Moore
 - output is a function of **present state only**


Example: Mealy and Moore Machines

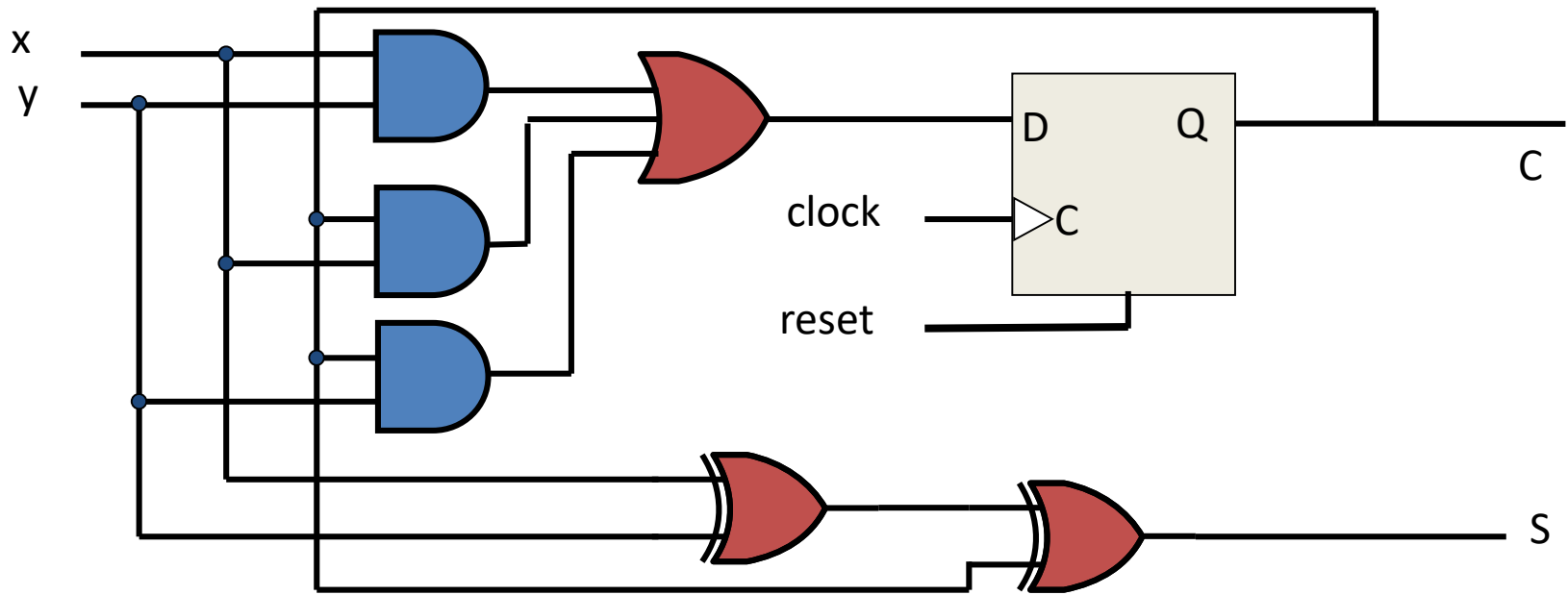

a Mealy machine

- External inputs x and y are asynchronous
- Thus, outputs may have momentary (incorrect) values
- Inputs must be synchronized with clocks
- Outputs must be sampled only during clock edges


Example: Moore Machines

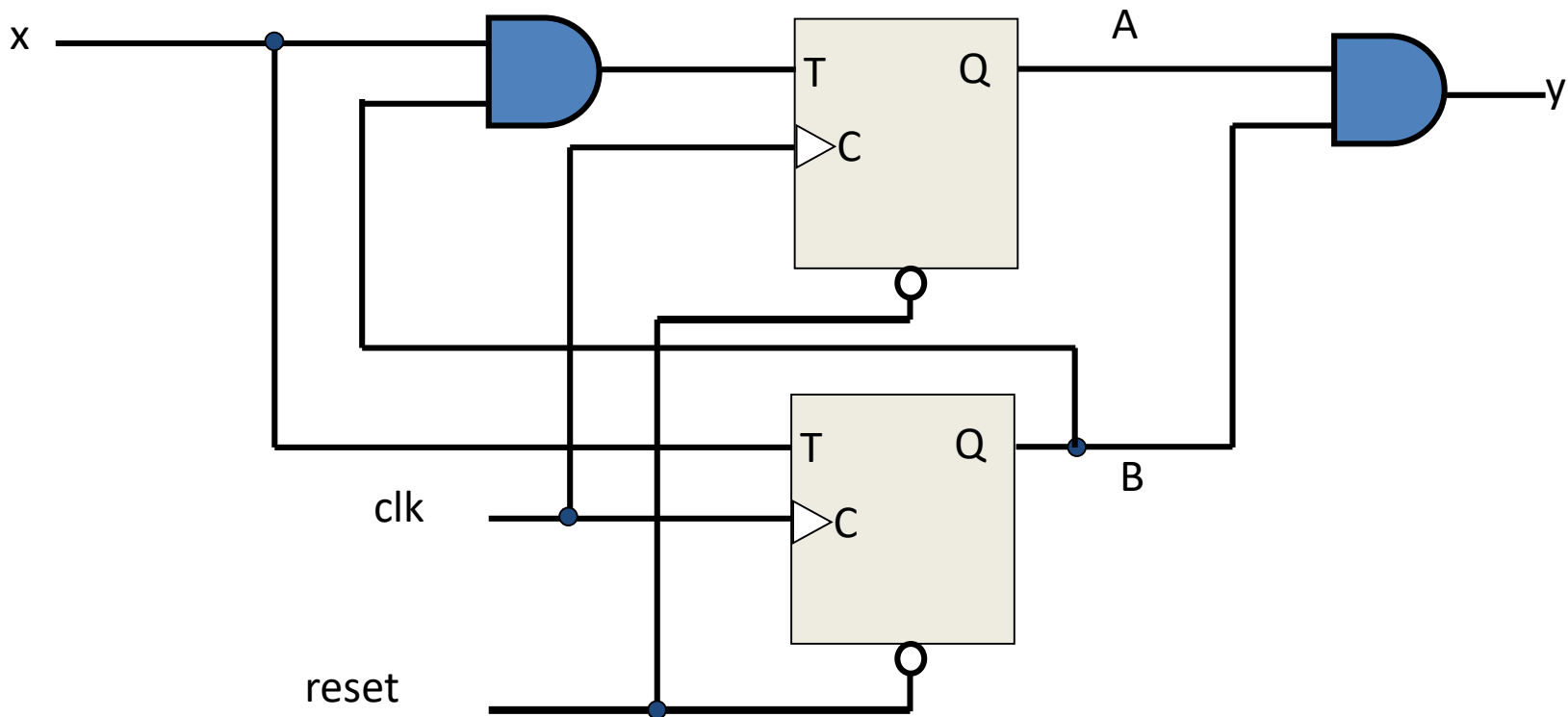

- Outputs are already synchronized with clock.
- They change synchronously with the clock edge.

Design Example - 1

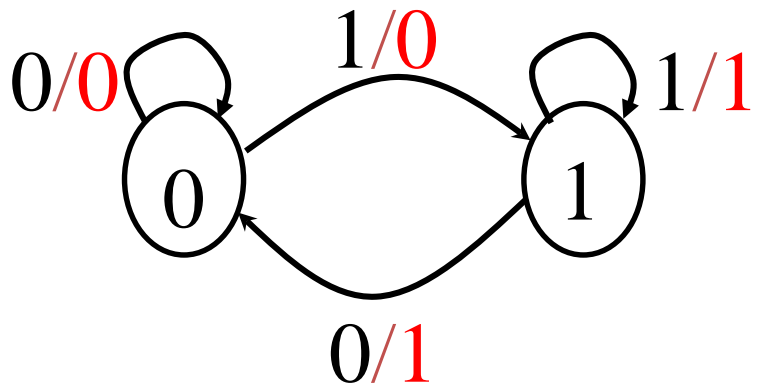
- Implement the following state diagram with D FFs.



x	Q(t)	Q(t+1)	D	Z
---	------	--------	---	---

Design Example - 1

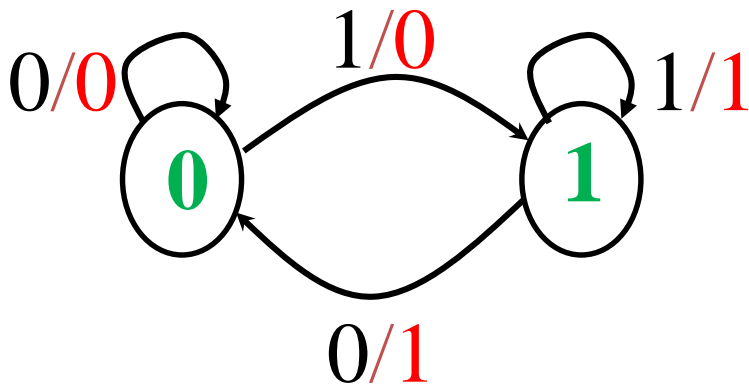
- Implement the following state diagram with D FFs.



x	Q(t)	Q(t+1)	D	Z
0	0	0		
0	1	1		
1	0	0		
1	1	1		

Design Example - 1

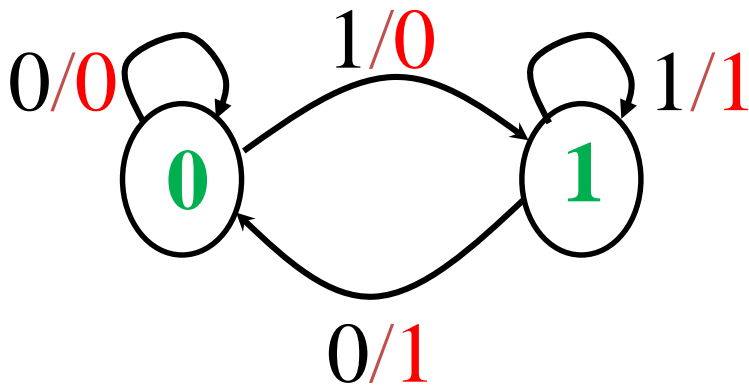
- Implement the following state diagram with D FFs.




x	Q(t)	Q(t+1)	D	Z
0	0	0		0
0	1	0		1
1	0	1		0
1	1	1		1

Design Example - 1

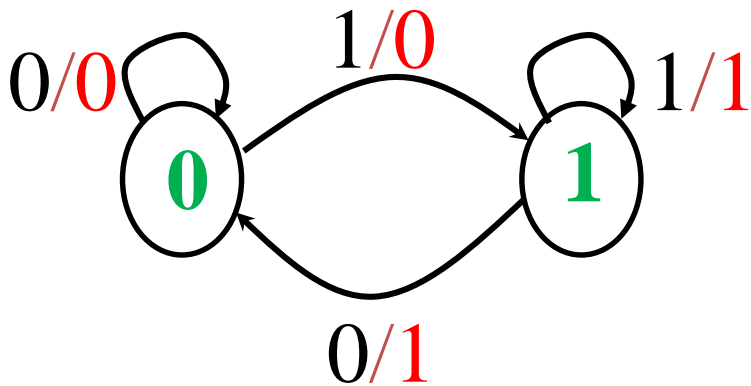- Implement the following state diagram with D FFs.



x	Q(t)	Q(t+1)	D	Z
0	0	0	0	0
0	1	0	0	1
1	0	1	1	0
1	1	1	1	1




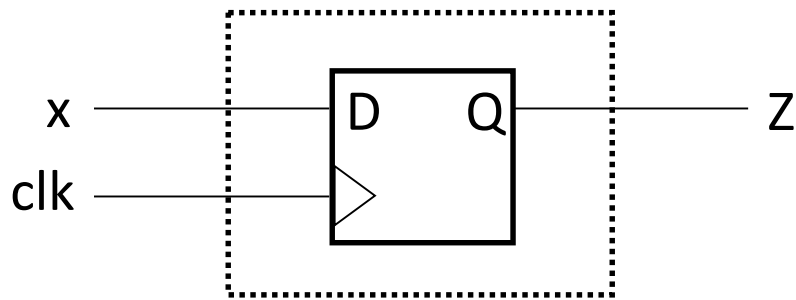


Design Example - 2

- Design a sequential circuit that counts up (00, 01, 10, 11, 00,...) when $x=1$, and counts down (00,11,10,01,00,...) when $x=0$. Use JK FFs.


Design Example - 2

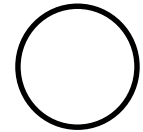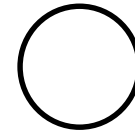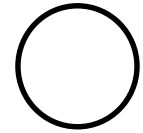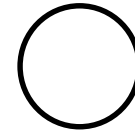- Design a sequential circuit
 - that counts up (00, 01, 10, 11, 00, ...) when $x=1$,
 - and counts down (00, 11, 10, 01, 00, ...) when $x=0$. Use JK FFs.




Design Example - 2

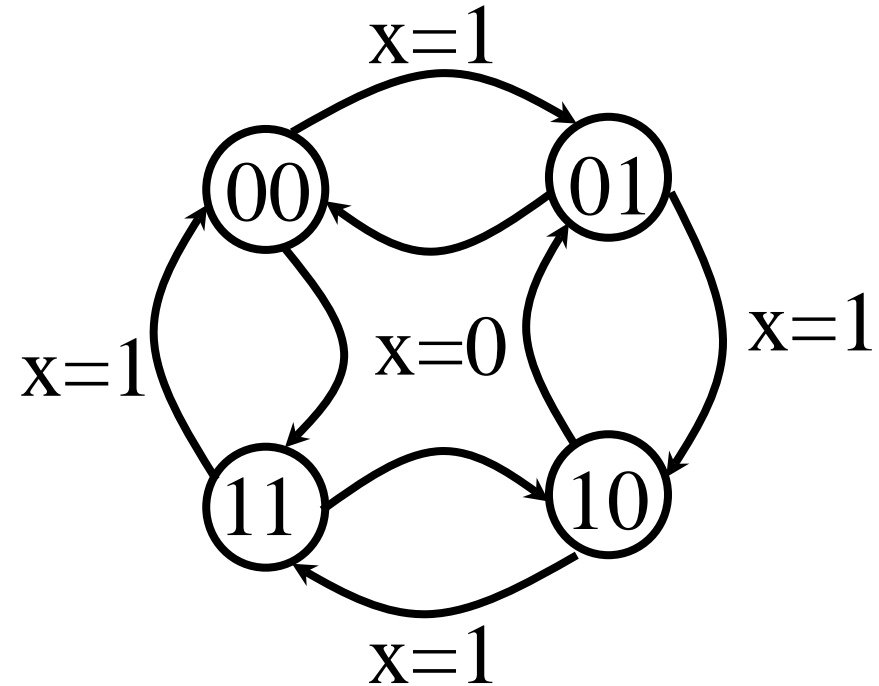- Design a sequential circuit
 - that counts up (00, 01, 10, 11, 00, ...) when $x=1$,
 - and counts down (00, 11, 10, 01, 00, ...) when $x=0$. Use JK FFs.




Design Example - 2

x	A	B	A(t+1)	B(t+1)	J _A	K _A	J _B	K _B

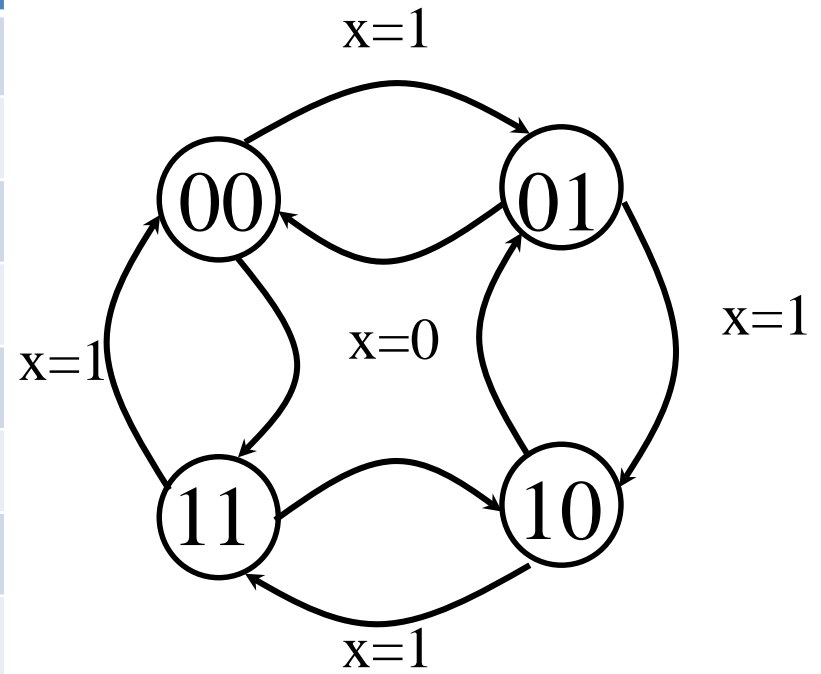


Design Example - 2

x	A	B	A(t+1)	B(t+1)	J _A	K _A	J _B	K _B
0	0	0						
0	0	1						
0	1	0						
0	1	1						
1	0	0						
1	0	1						
1	1	0						
1	1	1						

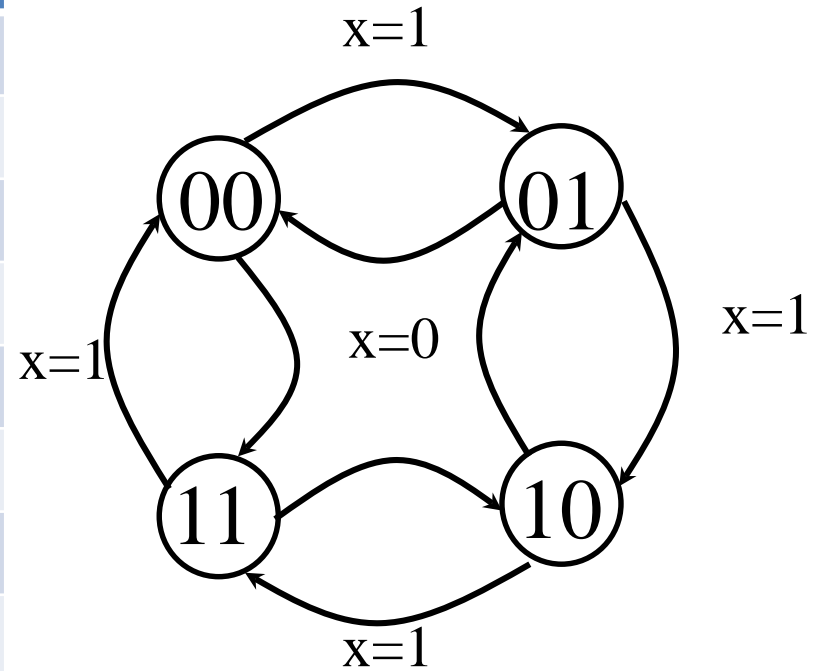


Design Example - 2

x	A	B	A(t+1)	B(t+1)	J _A	K _A	J _B	K _B
0	0	0	1	1				
0	0	1	0	0				
0	1	0	0	1				
0	1	1	1	0				
1	0	0	0	1				
1	0	1	1	0				
1	1	0	1	1				
1	1	1	0	0				

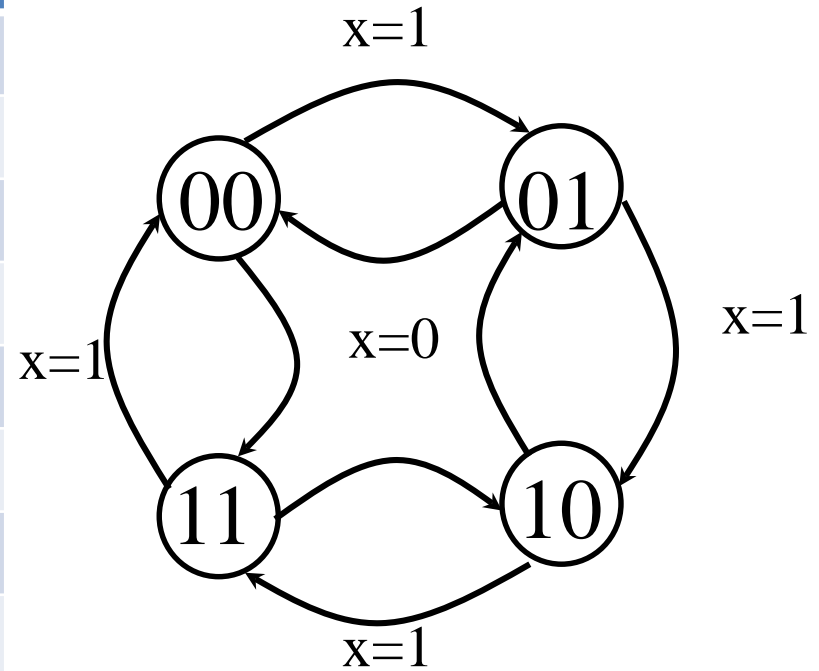

Design Example - 2

x	A	B	A(t+1)	B(t+1)	J _A	K _A	J _B	K _B
0	0	0	1	1				
0	0	1	0	0				
0	1	0	0	1				
0	1	1	1	0				
1	0	0	0	1				
1	0	1	1	0				
1	1	0	1	1				
1	1	1	0	0				

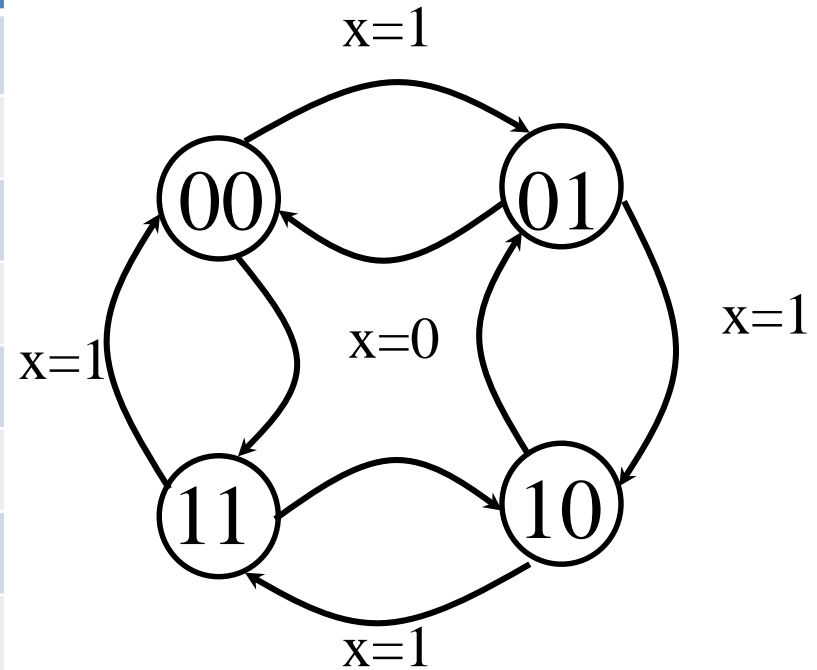


$$J = \begin{cases} Q(t+1) & Q(t)=0 \\ X & Q(t)=1 \end{cases}$$

$$K = \begin{cases} Q(t+1)' & Q(t)=1 \\ X & Q(t)=0 \end{cases}$$

Design Example - 2

x	A	B	A(t+1)	B(t+1)	J _A	K _A	J _B	K _B
0	0	0	1	1	1			
0	0	1	0	0	0			
0	1	0	0	1	X			
0	1	1	1	0	X			
1	0	0	0	1	0			
1	0	1	1	0	1			
1	1	0	1	1	X			
1	1	1	0	0	X			

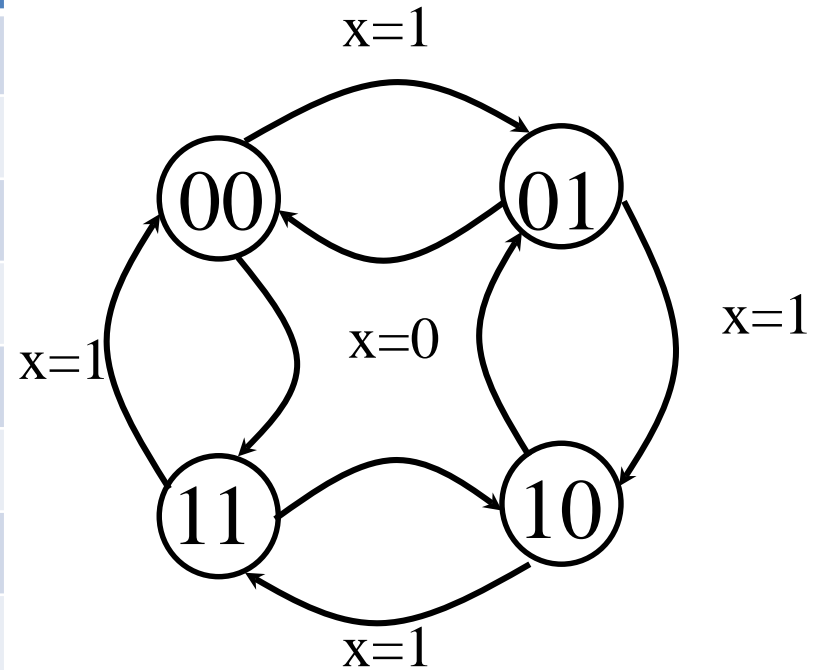


$$J = \begin{cases} Q(t+1) & Q(t)=0 \\ X & Q(t)=1 \end{cases}$$

$$K = \begin{cases} Q(t+1)' & Q(t)=1 \\ X & Q(t)=0 \end{cases}$$

Design Example - 2

x	A	B	A(t+1)	B(t+1)	J _A	K _A	J _B	K _B
0	0	0	1	1	1	X		
0	0	1	0	0	0	X		
0	1	0	0	1	X	1		
0	1	1	1	0	X	0		
1	0	0	0	1	0	X		
1	0	1	1	0	1	X		
1	1	0	1	1	X	0		
1	1	1	0	0	X	1		

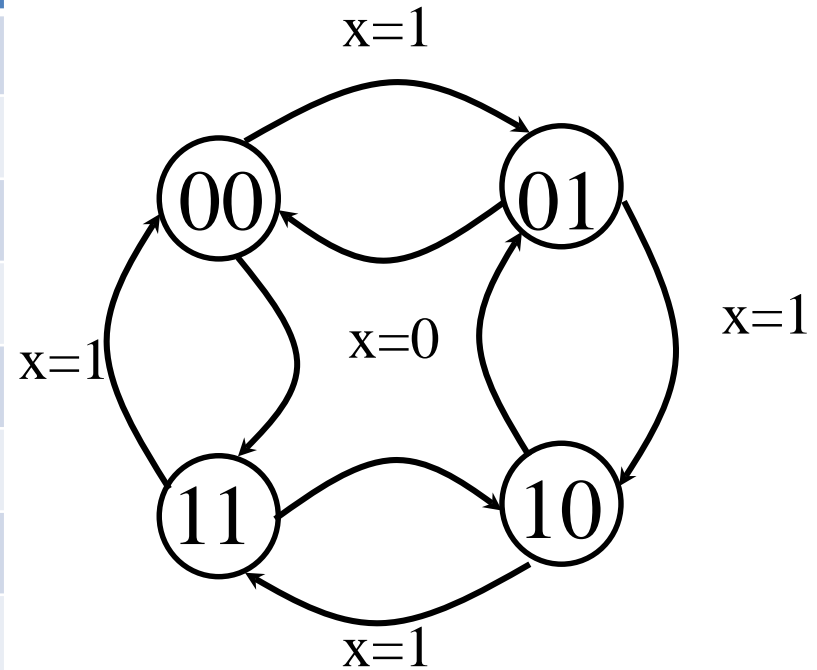


$$J = \begin{cases} Q(t+1) & Q(t)=0 \\ X & Q(t)=1 \end{cases}$$

$$K = \begin{cases} Q(t+1)' & Q(t)=1 \\ X & Q(t)=0 \end{cases}$$

Design Example - 2

x	A	B	A(t+1)	B(t+1)	J _A	K _A	J _B	K _B
0	0	0	1	1	1	X	1	
0	0	1	0	0	0	X	X	
0	1	0	0	1	X	1	1	
0	1	1	1	0	X	0	X	
1	0	0	0	1	0	X	1	
1	0	1	1	0	1	X	X	
1	1	0	1	1	X	0	1	
1	1	1	0	0	X	1	X	

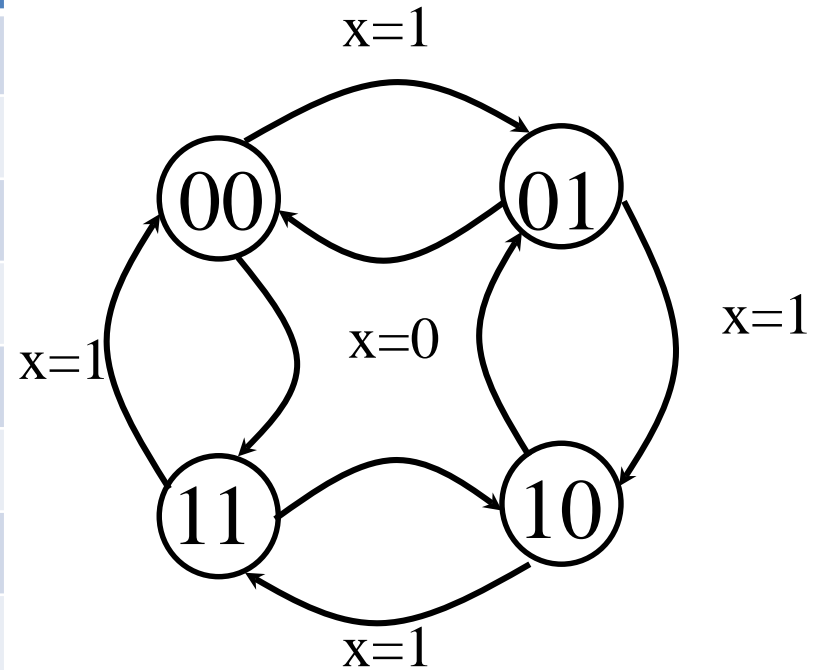


$$J = \begin{cases} Q(t+1) & Q(t)=0 \\ X & Q(t)=1 \end{cases}$$

$$K = \begin{cases} Q(t+1)' & Q(t)=1 \\ X & Q(t)=0 \end{cases}$$

Design Example - 2

x	A	B	A(t+1)	B(t+1)	J _A	K _A	J _B	K _B
0	0	0	1	1	1	X	1	X
0	0	1	0	0	0	X	X	1
0	1	0	0	1	X	1	1	X
0	1	1	1	0	X	0	X	1
1	0	0	0	1	0	X	1	X
1	0	1	1	0	1	X	X	1
1	1	0	1	1	X	0	1	X
1	1	1	0	0	X	1	X	1

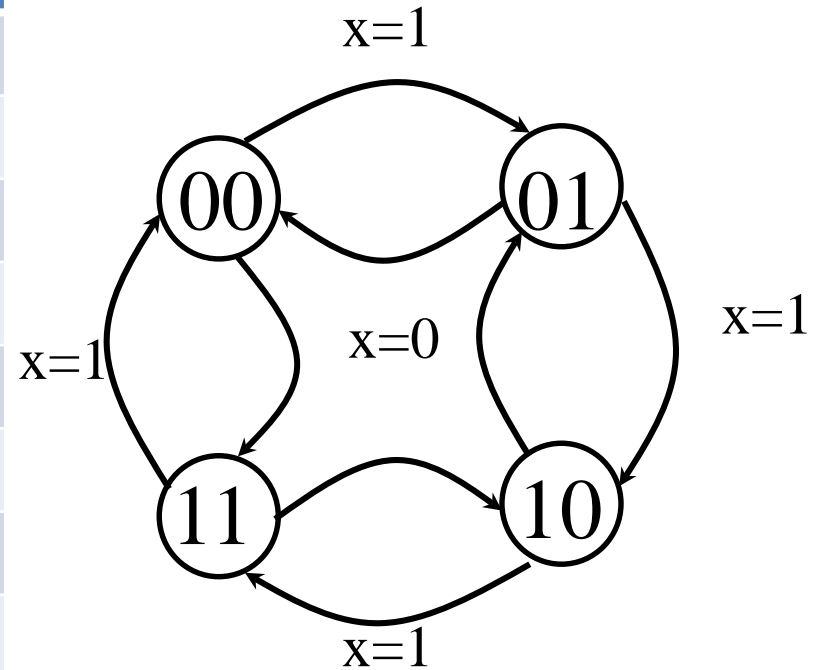


$$J = \begin{cases} Q(t+1) & Q(t)=0 \\ X & Q(t)=1 \end{cases}$$

$$K = \begin{cases} Q(t+1)' & Q(t)=1 \\ X & Q(t)=0 \end{cases}$$

Design Example - 2

x	A	B	A(t+1)	B(t+1)	J _A	K _A	J _B	K _B
0	0	0	1	1	1	X	1	X
0	0	1	0	0	0	X	X	1
0	1	0	0	1	X	1	1	X
0	1	1	1	0	X	0	X	1
1	0	0	0	1	0	X	1	X
1	0	1	1	0	1	X	X	1
1	1	0	1	1	X	0	1	X
1	1	1	0	0	X	1	X	1

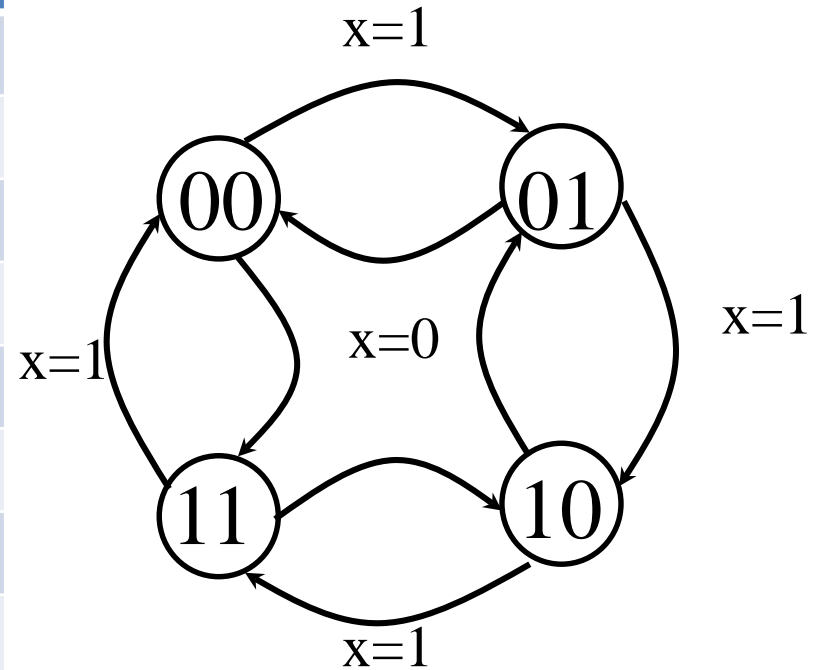

$$J_A = ?$$


$$J_B = ?$$

$$K_A = ?$$

$$K_B = ?$$

Design Example - 2

x	A	B	A(t+1)	B(t+1)	J _A	K _A	J _B	K _B
0	0	0	1	1	1	X	1	X
0	0	1	0	0	0	X	X	1
0	1	0	0	1	X	1	1	X
0	1	1	1	0	X	0	X	1
1	0	0	0	1	0	X	1	X
1	0	1	1	0	1	X	X	1
1	1	0	1	1	X	0	1	X
1	1	1	0	0	X	1	X	1

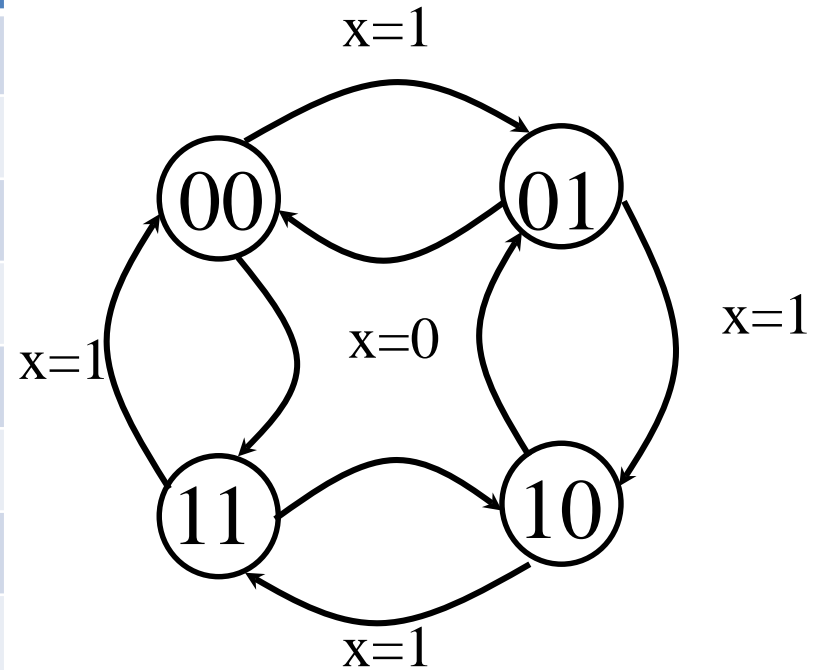


AB		x			
		00	01	11	10
x	0	1	0	X	X
	1	0	1	X	X

AB		x			
		00	01	11	10
x	0	X	X	0	1
	1	X	X	1	0

Design Example - 2


- $J_A = xB + x'B'$
- $K_A = xB + x'B'$
- $J_B = 1$
- $K_B = 1$
- **Let's draw the circuit**

Design Example - 3

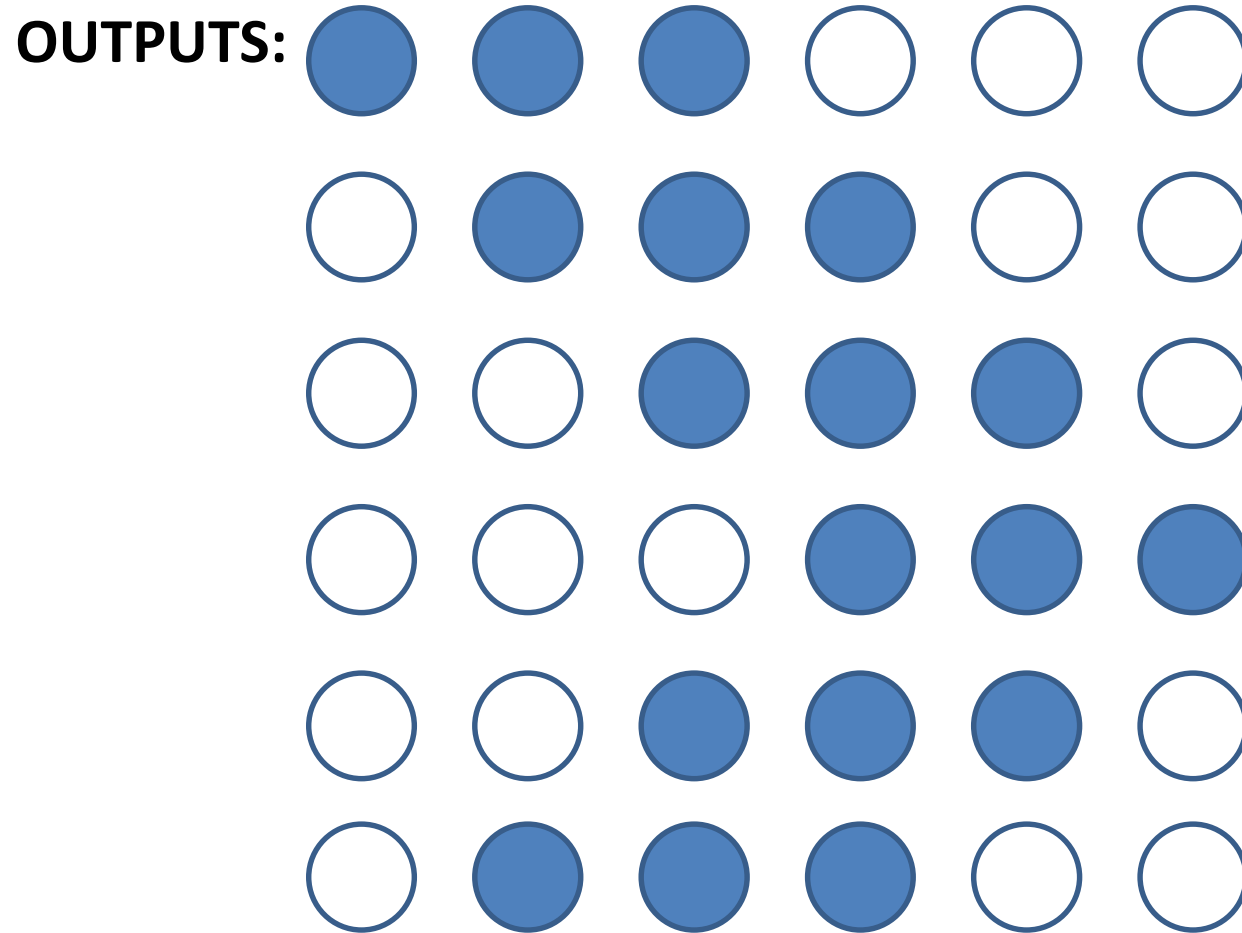

**design
with JK
flip-flops**

STATE TRANSITIONS:

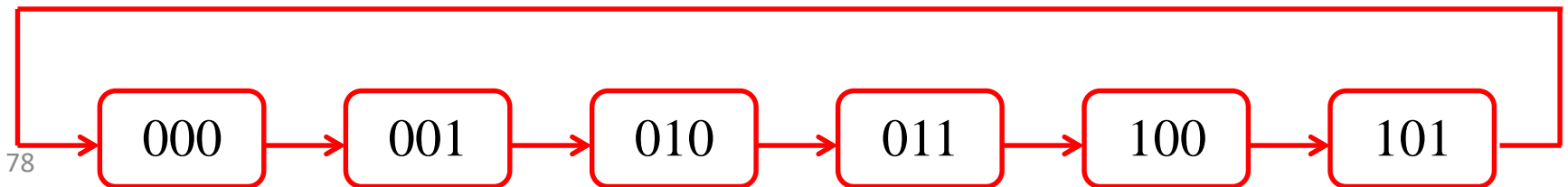

Design Example - 3

A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
						1	1	1	0	0	0						
						0	1	1	1	0	0						
						0	0	1	1	1	0						
						0	0	0	1	1	1						
						0	0	1	1	1	0						
						0	1	1	1	0	0						


$$J = \begin{cases} Q(t+1) \\ X \end{cases}$$

$$\begin{matrix} Q(t)=0 \\ Q(t)=1 \end{matrix}$$

$$K = \begin{cases} Q(t+1)' \\ X \end{cases}$$

$$\begin{matrix} Q(t)=1 \\ Q(t)=0 \end{matrix}$$

Mealy or Moore?

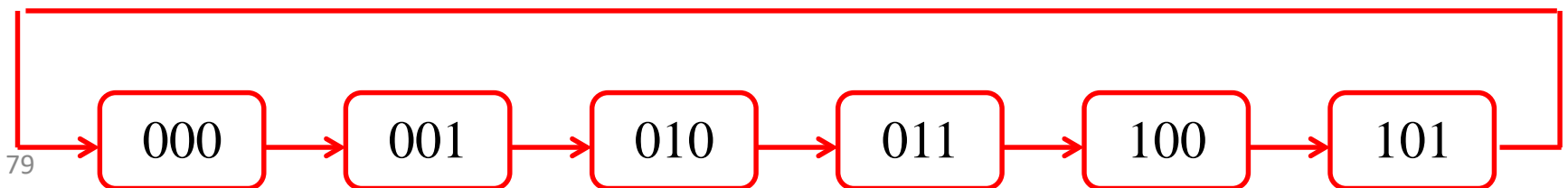

Design Example - 3


A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	1	1	0	0	0						
0	0	1	0	1	0	0	1	1	1	0	0						
0	1	0	0	1	1	0	0	1	1	1	0						
0	1	1	1	0	0	0	0	0	1	1	1						
1	0	0	1	0	1	0	0	1	1	1	0						
1	0	1	0	0	0	0	1	1	1	0	0						

$$J = \begin{cases} Q(t+1) \\ X \end{cases}$$

$$\begin{aligned} Q(t) &= 0 \\ Q(t) &= 1 \end{aligned}$$

$$K = \begin{cases} Q(t+1)' \\ X \end{cases}$$
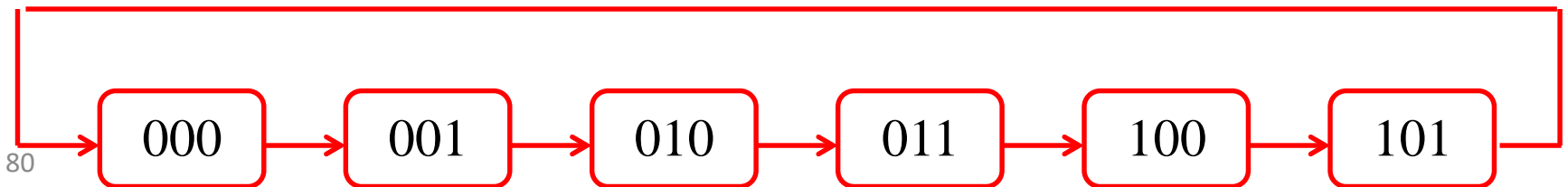
$$\begin{aligned} Q(t) &= 1 \\ Q(t) &= 0 \end{aligned}$$



Design Example - 3


A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	1	1	0	0	0	0		0		1	
0	0	1	0	1	0	0	1	1	1	0	0	0		1			
0	1	0	0	1	1	0	0	1	1	1	0	0				1	
0	1	1	1	0	0	0	0	0	1	1	1	1					
1	0	0	1	0	1	0	0	1	1	1	0			0		1	
1	0	1	0	0	0	0	1	1	1	0	0			0			

$$J = \begin{cases} Q(t+1) \\ X \end{cases}$$

$$\begin{matrix} Q(t)=0 \\ Q(t)=1 \end{matrix}$$

$$K = \begin{cases} Q(t+1)' \\ X \end{cases}$$
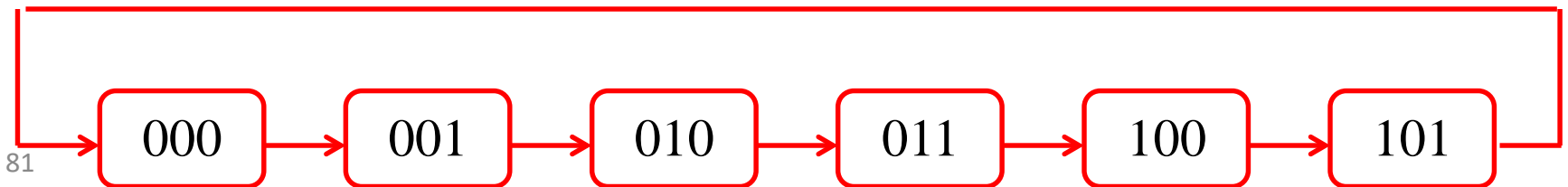
$$\begin{matrix} Q(t)=1 \\ Q(t)=0 \end{matrix}$$



Design Example - 3


A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	1	1	0	0	0	0		0		1	
0	0	1	0	1	0	0	1	1	1	0	0	0		1		X	
0	1	0	0	1	1	0	0	1	1	1	0	0		X		1	
0	1	1	1	0	0	0	0	0	1	1	1	1		X		X	
1	0	0	1	0	1	0	0	1	1	1	0	X		0		1	
1	0	1	0	0	0	0	1	1	1	0	0	X		0		X	

$$J = \begin{cases} Q(t+1) \\ X \end{cases}$$

$$\begin{matrix} Q(t)=0 \\ Q(t)=1 \end{matrix}$$

$$K = \begin{cases} Q(t+1)' \\ X \end{cases}$$
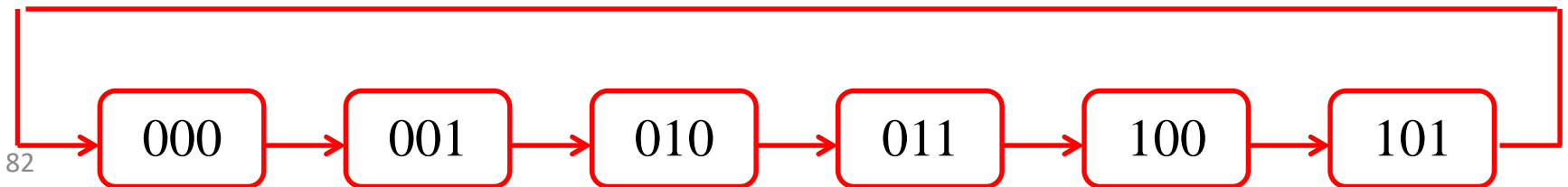
$$\begin{matrix} Q(t)=1 \\ Q(t)=0 \end{matrix}$$



Design Example - 3


A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	1	1	0	0	0	0		0		1	
0	0	1	0	1	0	0	1	1	1	0	0	0		1		X	1
0	1	0	0	1	1	0	0	1	1	1	0	0		X	0	1	
0	1	1	1	0	0	0	0	0	1	1	1	1		X	1	X	1
1	0	0	1	0	1	0	0	1	1	1	0	X	0	0		1	
1	0	1	0	0	0	0	1	1	1	0	0	X	1	0		X	1

$$J = \begin{cases} Q(t+1) \\ X \end{cases}$$

$$\begin{aligned} Q(t) &= 0 \\ Q(t) &= 1 \end{aligned}$$

$$K = \begin{cases} Q(t+1)' \\ X \end{cases}$$
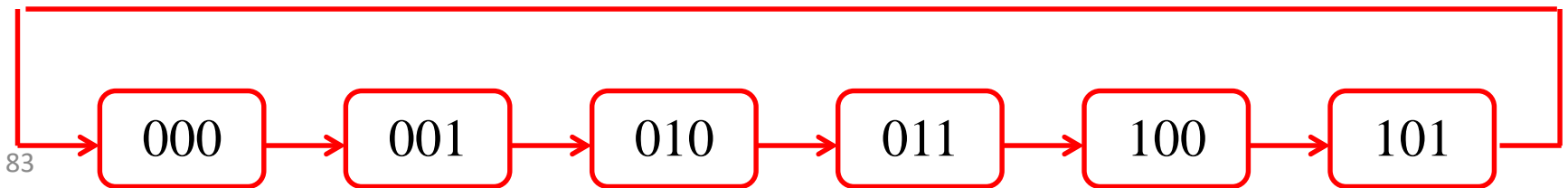
$$\begin{aligned} Q(t) &= 1 \\ Q(t) &= 0 \end{aligned}$$



Design Example - 3


A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	1	1	0	0	0	0	X	0	X	1	X
0	0	1	0	1	0	0	1	1	1	0	0	0	X	1	X	X	1
0	1	0	0	1	1	0	0	1	1	1	0	0	X	X	0	1	X
0	1	1	1	0	0	0	0	0	1	1	1	1	X	X	1	X	1
1	0	0	1	0	1	0	0	1	1	1	0	X	0	0	X	1	X
1	0	1	0	0	0	0	1	1	1	0	0	X	1	0	X	X	1

$$J = \begin{cases} Q(t+1) \\ X \end{cases}$$

$$\begin{matrix} Q(t)=0 \\ Q(t)=1 \end{matrix}$$

$$K = \begin{cases} Q(t+1)' \\ X \end{cases}$$
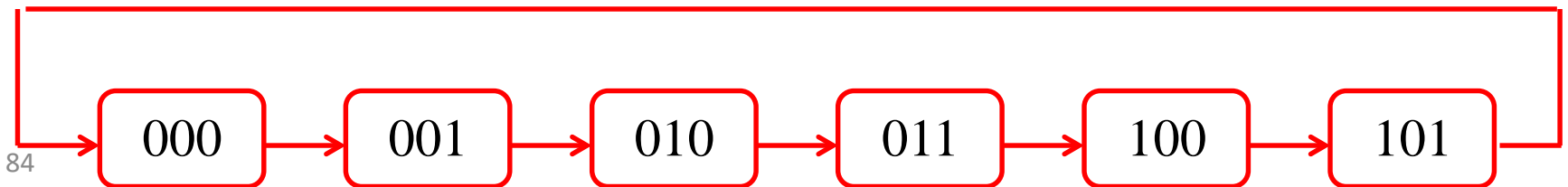
$$\begin{matrix} Q(t)=1 \\ Q(t)=0 \end{matrix}$$



Design Example - 3

A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	1	1	0	0	0	0	X	0	X	1	X
0	0	1	0	1	0	0	1	1	1	0	0	0	X	1	X	X	1
0	1	0	0	1	1	0	0	1	1	1	0	0	X	X	0	1	X
0	1	1	1	0	0	0	0	0	1	1	1	1	X	X	1	X	1
1	0	0	1	0	1	0	0	1	1	1	0	X	0	0	X	1	X
1	0	1	0	0	0	0	1	1	1	0	0	X	1	0	X	X	1
1	1	0										X	X	X	X	X	X
1	1	1										X	X	X	X	X	X

		BC			
		00	01	11	10
A	0	0	0	1	0
	1	X	X	X	X

$J_A =$

		BC			
		00	01	11	10
A	0	X	X	X	X
	1	0	1	X	X

$K_A =$

Design Example - 3

A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	1	1	0	0	0	0	X	0	X	1	X
0	0	1	0	1	0	0	1	1	1	0	0	0	X	1	X	X	1
0	1	0	0	1	1	0	0	1	1	1	0	0	X	X	0	1	X
0	1	1	1	0	0	0	0	0	1	1	1	1	X	X	1	X	1
1	0	0	1	0	1	0	0	1	1	1	0	X	0	0	X	1	X
1	0	1	0	0	0	0	1	1	1	0	0	X	1	0	X	X	1
1	1	0										X	X	X	X	X	X
1	1	1										X	X	X	X	X	X

		BC			
		00	01	11	10
A	0	0	0	1	0
	1	X	X	X	X

$$J_A = BC$$

		BC			
		00	01	11	10
A	0	X	X	X	X
	1	0	1	X	X

$$K_A = C$$

Design Example - 3

A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	1	1	0	0	0	0	X	0	X	1	X
0	0	1	0	1	0	0	1	1	1	0	0	0	X	1	X	X	1
0	1	0	0	1	1	0	0	1	1	1	0	0	X	X	0	1	X
0	1	1	1	0	0	0	0	0	1	1	1	1	X	X	1	X	1
1	0	0	1	0	1	0	0	1	1	1	0	X	0	0	X	1	X
1	0	1	0	0	0	0	1	1	1	0	0	X	1	0	X	X	1
1	1	0										X	X	X	X	X	X
1	1	1										X	X	X	X	X	X

		BC			
		00	01	11	10
A	0	0	1	X	X
	1	0	0	X	X

$J_B =$

		BC			
		00	01	11	10
A	0	X	X	1	0
	1	X	X	X	X

$K_B =$

Design Example - 3

A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	1	1	0	0	0	0	X	0	X	1	X
0	0	1	0	1	0	0	1	1	1	0	0	0	X	1	X	X	1
0	1	0	0	1	1	0	0	1	1	1	0	0	X	X	0	1	X
0	1	1	1	0	0	0	0	0	1	1	1	1	X	X	1	X	1
1	0	0	1	0	1	0	0	1	1	1	0	X	0	0	X	1	X
1	0	1	0	0	0	0	1	1	1	0	0	X	1	0	X	X	1
1	1	0										X	X	X	X	X	X
1	1	1										X	X	X	X	X	X

		BC			
		00	01	11	10
A	0	0	1	X	X
	1	0	0	X	X

$$J_B = A'C$$

		BC			
		00	01	11	10
A	0	X	X	1	0
	1	X	X	X	X

$$K_B = C$$

Design Example - 3

A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	1	1	0	0	0	0	X	0	X	1	X
0	0	1	0	1	0	0	1	1	1	0	0	0	X	1	X	X	1
0	1	0	0	1	1	0	0	1	1	1	0	0	X	X	0	1	X
0	1	1	1	0	0	0	0	0	1	1	1	1	X	X	1	X	1
1	0	0	1	0	1	0	0	1	1	1	0	X	0	0	X	1	X
1	0	1	0	0	0	0	1	1	1	0	0	X	1	0	X	X	1
1	1	0										X	X	X	X	X	X
1	1	1										X	X	X	X	X	X

		BC			
		00	01	11	10
A	0	1	X	1	X
	1	1	X	X	X

J_C=

		BC			
		00	01	11	10
A	0	X	1	1	X
	1	X	1	X	X

K_C=

Design Example - 3

A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	1	1	0	0	0	0	X	0	X	1	X
0	0	1	0	1	0	0	1	1	1	0	0	0	X	1	X	X	1
0	1	0	0	1	1	0	0	1	1	1	0	0	X	X	0	1	X
0	1	1	1	0	0	0	0	0	1	1	1	1	X	X	1	X	1
1	0	0	1	0	1	0	0	1	1	1	0	X	0	0	X	1	X
1	0	1	0	0	0	0	1	1	1	0	0	X	1	0	X	X	1
1	1	0										X	X	X	X	X	X
1	1	1										X	X	X	X	X	X




		BC			
		00	01	11	10
A	0	1	X	1	X
	1	1	X	X	X

$J_C=1$

		BC			
		00	01	11	10
A	0	X	1	1	X
	1	X	1	X	X

$K_C=1$

Design Example - 3

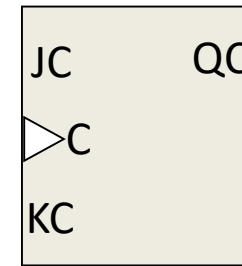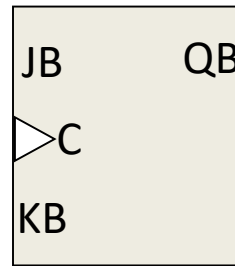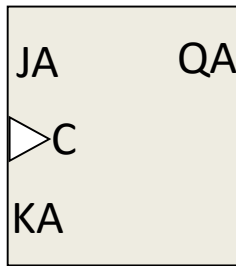

**We can also solve for outputs z1-z6
by looking at K-maps of A(t),B(t),C(t)**

Design Example - 3

A(t)	B(t)	C(t)	A (t+1)	B (t+1)	C (t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	1	1	0	0	0	0	0	0	0	1	1
0	0	1	0	1	0	0	1	1	1	0	0	0	1	1	1	1	1
0	1	0	0	1	1	0	0	1	1	1	0	0	0	0	0	1	1
0	1	1	1	0	0	0	0	0	1	1	1	1	1	1	1	1	1
1	0	0	1	0	1	0	0	1	1	1	0	0	0	0	0	1	1
1	0	1	0	0	0	0	1	1	1	0	0	0	1	0	1	1	1
1	1	0															
1	1	1															

$$J_A = BC$$

$$J_B = A'C$$

$$J_C = 1$$

$$K_A = C$$

$$K_B = C$$

$$K_C = 1$$

Design Example - 3

A(t)	B(t)	C(t)	A (t+1)	B (t+1)	C (t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	1	1	0	0	0	0	0	0	0	1	1
0	0	1	0	1	0	0	1	1	1	0	0	0	1	1	1	1	1
0	1	0	0	1	1	0	0	1	1	1	0	0	0	0	0	1	1
0	1	1	1	0	0	0	0	0	1	1	1	1	1	1	1	1	1
1	0	0	1	0	1	0	0	1	1	1	0	0	0	0	0	1	1
1	0	1	0	0	0	0	1	1	1	0	0	0	1	0	1	1	1
1	1	0										0	0	0	0	1	1
1	1	1										1	1	0	1	1	1

$$J_A = BC$$

$$J_B = A'C$$

$$J_C = 1$$

$$K_A = C$$

$$K_B = C$$

$$K_C = 1$$

Design Example - 3

A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	1	1	0	0	0	0	0	0	0	1	1
0	0	1	0	1	0	0	1	1	1	0	0	0	1	1	1	1	1
0	1	0	0	1	1	0	0	1	1	1	0	0	0	0	0	1	1
0	1	1	1	0	0	0	0	0	1	1	1	1	1	1	1	1	1
1	0	0	1	0	1	0	0	1	1	1	0	0	0	0	0	1	1
1	0	1	0	0	0	0	1	1	1	0	0	0	1	0	1	1	1
1	1	0	1	1	1							0	0	0	0	1	1
1	1	1	0	0	0							1	1	0	1	1	1

$$J_A = BC$$

$$A(t+1) = BCA' + C'A$$

$$K_A = C$$

$$J_B = A'C$$

$$B(t+1) = A'CB' + C'B$$

$$K_B = C$$


$$J_C = 1$$

$$C(t+1) = C'$$

$$K_C = 1$$

Design Example - 3

A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	1	1	0	0	0	0	0	0	0	1	1
0	0	1	0	1	0	0	1	1	1	0	0	0	1	1	1	1	1
0	1	0	0	1	1	0	0	1	1	1	0	0	0	0	0	1	1
0	1	1	1	0	0	0	0	0	1	1	1	1	1	1	1	1	1
1	0	0	1	0	1	0	0	1	1	1	0	0	0	0	0	1	1
1	0	1	0	0	0	0	1	1	1	0	0	0	1	0	1	1	1
1	1	0	1	1	1							0	0	0	0	1	1
1	1	1	0	0	0							1	1	0	1	1	1

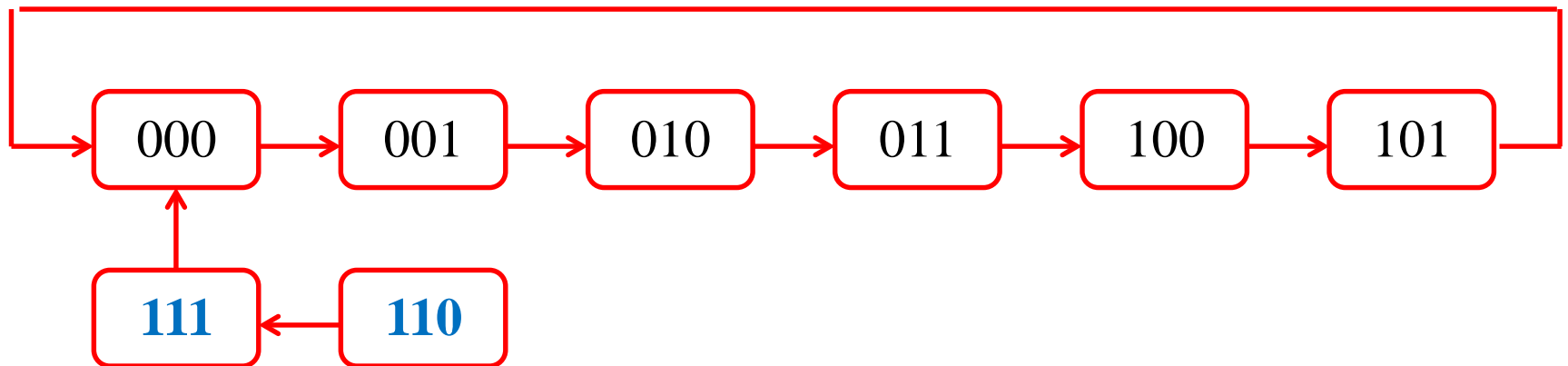

Design Example - 3

- now let's redo the design with D FFs

Design Example - 3

A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	DA	DB	DC
0	0	0	0	0	1	1	1	1	0	0	0			
0	0	1	0	1	0	0	1	1	1	0	0			
0	1	0	0	1	1	0	0	1	1	1	0			
0	1	1	1	0	0	0	0	0	1	1	1			
1	0	0	1	0	1	0	0	1	1	1	0			
1	0	1	0	0	0	0	1	1	1	0	0			
1	1	0	1	1	1									
1	1	1	0	0	0									

$$A(t+1) = BCA' + C'A =$$

$$B(t+1) = A'CB' + C'B =$$

$$C(t+1) = C' =$$

Design Example - 3

A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	DA	DB	DC
0	0	0	0	0	1	1	1	1	0	0	0			
0	0	1	0	1	0	0	1	1	1	0	0			
0	1	0	0	1	1	0	0	1	1	1	0			
0	1	1	1	0	0	0	0	0	1	1	1			
1	0	0	1	0	1	0	0	1	1	1	0			
1	0	1	0	0	0	0	1	1	1	0	0			
1	1	0	1	1	1									
1	1	1	0	0	0									

$$A(t+1) = BCA' + C'A = D_A$$

$$B(t+1) = A'CB' + C'B = D_B$$

$$C(t+1) = C' = D_C$$

Design Example - 3

A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	z1	z2	z3	z4	z5	z6	DA	DB	DC
0	0	0	0	0	1	1	1	1	0	0	0			1
0	0	1	0	1	0	0	1	1	1	0	0		1	
0	1	0	0	1	1	0	0	1	1	1	0		1	1
0	1	1	1	0	0	0	0	0	1	1	1	1		
1	0	0	1	0	1	0	0	1	1	1	0	1		1
1	0	1	0	0	0	0	1	1	1	0	0			
1	1	0	1	1	1							1	1	1
1	1	1	0	0	0									

$$A(t+1) = BCA' + C'A = D_A$$

$$B(t+1) = A'CB' + C'B = D_B$$

$$C(t+1) = C' = D_C$$






Design Example - 4

- Design a logic circuit with JK flip-flops that detects the sequence 1011 and outputs 1 in that case, 0 otherwise.






Design Example - 4

?

Design Example - 4

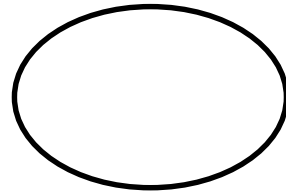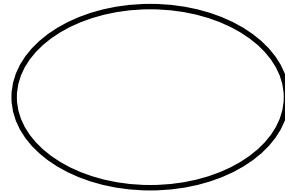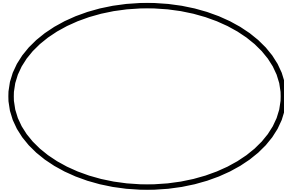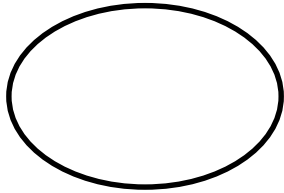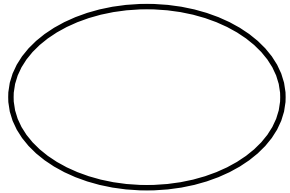

Design Example - 4

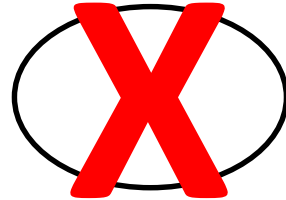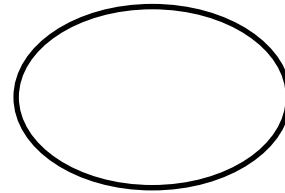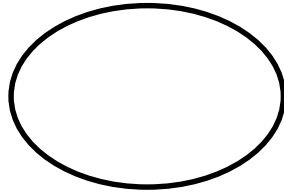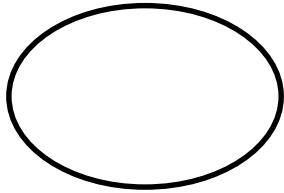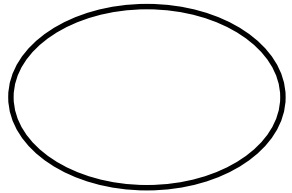

Design Example - 4

I.C.

1

10

101

Design Example - 4

consider the sequence:

00100101011011001

consider the sequence:

00100101011011001


I.C. (0)

1

10


101

Design Example - 4

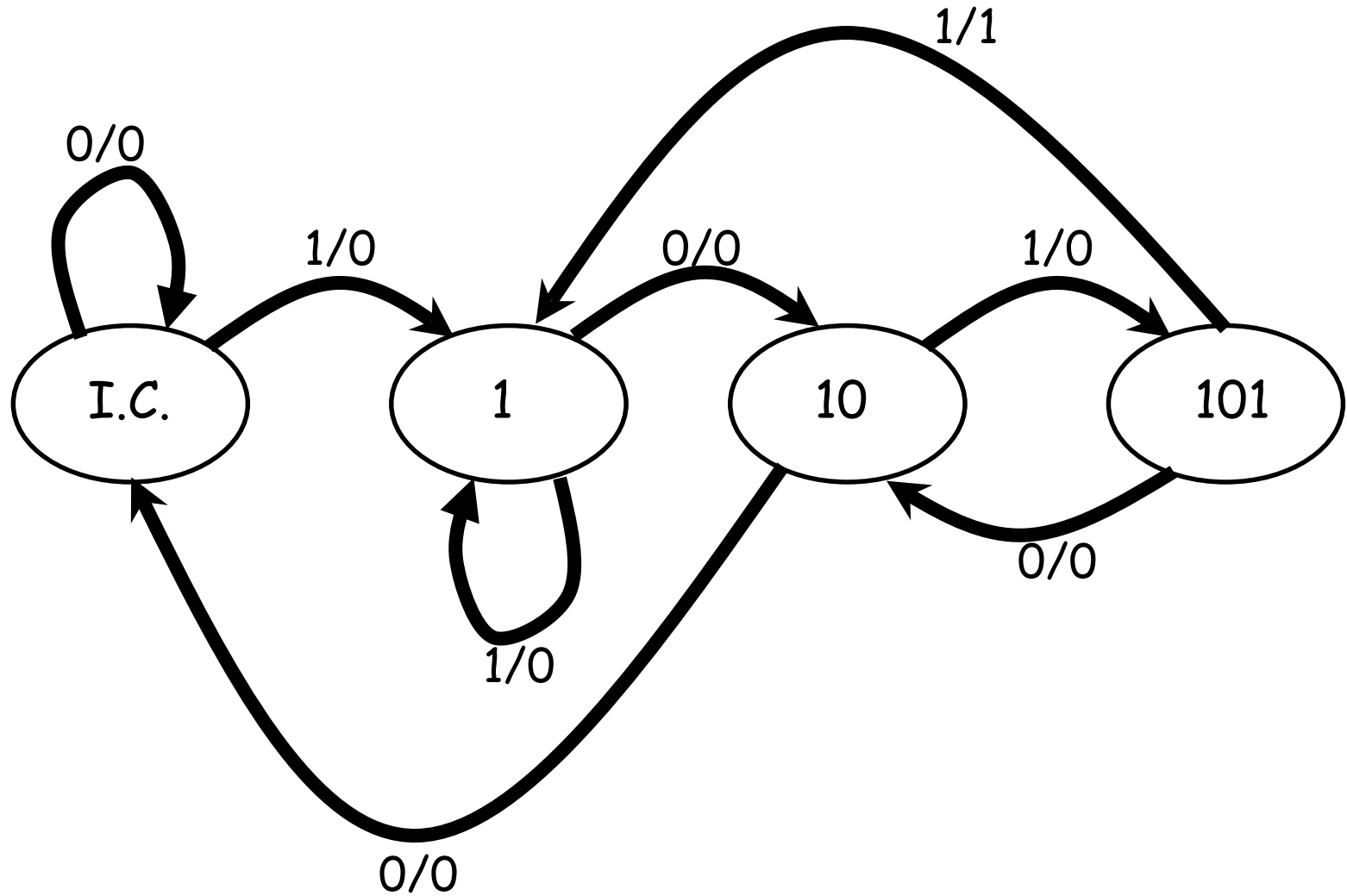

Design Example - 4

now we represent with **states**

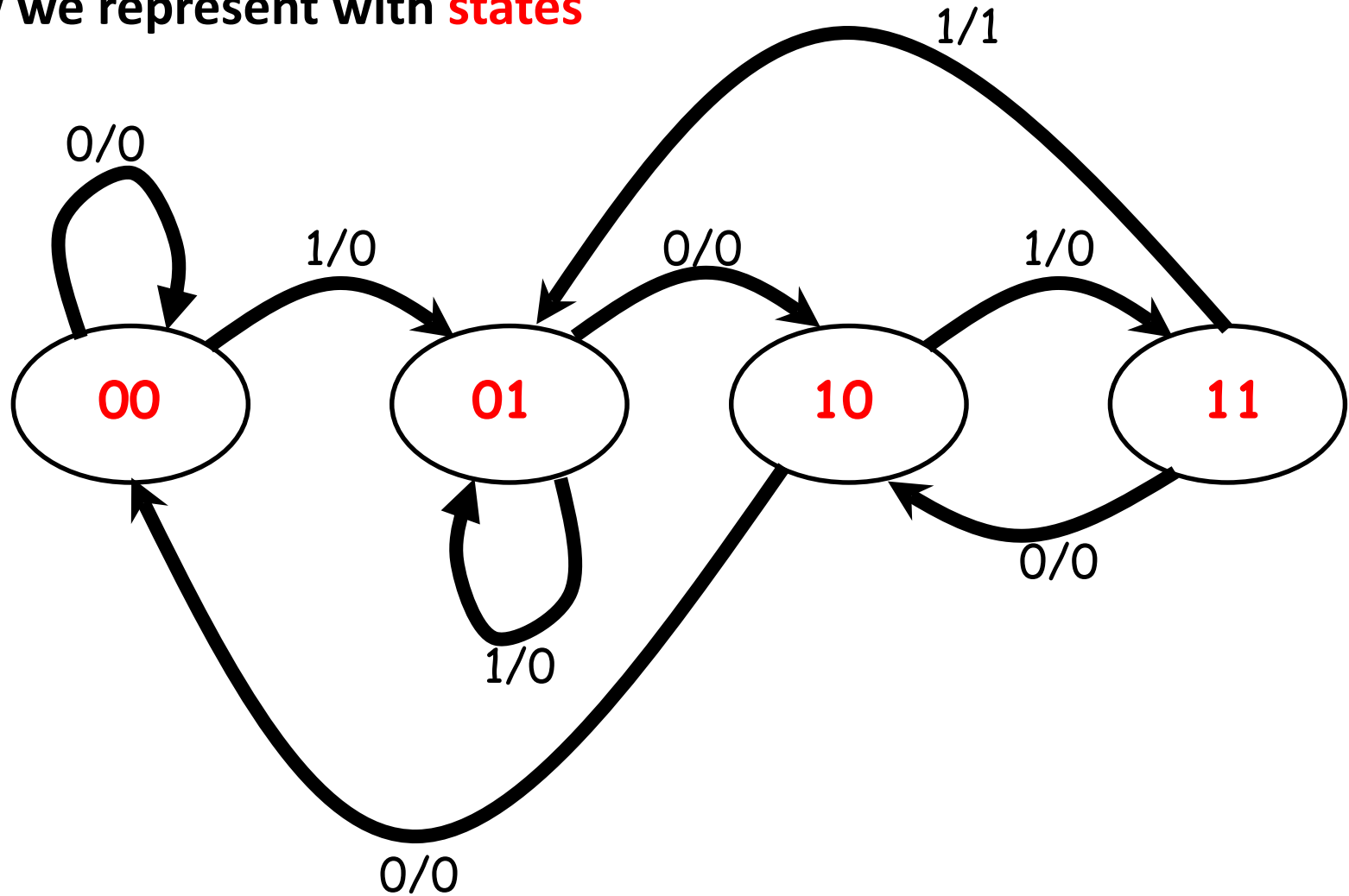

Design Example - 4

$x(t)$	$A(t)$	$B(t)$	$A(t+1)$	$B(t+1)$	Z	J_A	K_A	J_B	K_B

Design Example - 4

$x(t)$	$A(t)$	$B(t)$	A $(t+1)$	B $(t+1)$	Z	J_A	K_A	J_B	K_B
0	0	0	0	0	0				
0	0	1	1	0	0				
0	1	0	0	0	0				
0	1	1	1	0	0				
1	0	0	0	1	0				
1	0	1	0	1	0				
1	1	0	1	1	0				
1	1	1	0	1	1				

Design Example - 4

$x(t)$	$A(t)$	$B(t)$	A (t+1)	B (t+1)	Z	J_A	K_A	J_B	K_B
0	0	0	0	0	0	0	X	0	X
0	0	1	1	0	0	1	X	X	1
0	1	0	0	0	0	X	1	0	X
0	1	1	1	0	0	X	0	X	1
1	0	0	0	1	0	0	X	1	X
1	0	1	0	1	0	0	X	X	0
1	1	0	1	1	0	X	0	1	X
1	1	1	0	1	1	X	1	X	0

Design Example - 4

	AB			
x	00	01	11	10
0				
1				

$J_A =$

	AB			
x	00	01	11	10
0				
1				

$K_A =$

	AB			
x	00	01	11	10
0				
1				

$J_B =$

	AB			
x	00	01	11	10
0				
1				

$K_B =$

Design Example - 4

	AB			
x	00	01	11	10
0	0	1	X	X
1	0	0	X	X

$$J_A = X'B$$

	AB			
x	00	01	11	10
0	X	X	0	1
1	X	X	1	0

$$K_A = XB + X'B'$$



	AB			
x	00	01	11	10
0	0	X	X	0
1	1	X	X	1

$$J_B = X$$

	AB			
x	00	01	11	10
0	X	1	1	X
1	X	0	0	X

$$K_B = X'$$

Design Example - 4

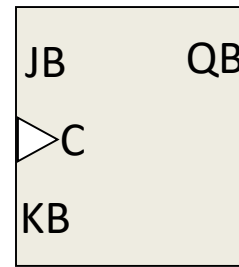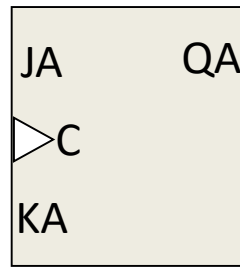

Design Example - 4

